

Generator Third-Harmonic Protection Explained


Ritwik Chowdhury, Dale Finney,
Normann Fischer, and Jason Young
Schweitzer Engineering Laboratories, Inc.

© 2018 SEL


Overview

- Third-harmonic schemes
- Security and settings
- Sensitivity and coverage

Third-Harmonic Circuit

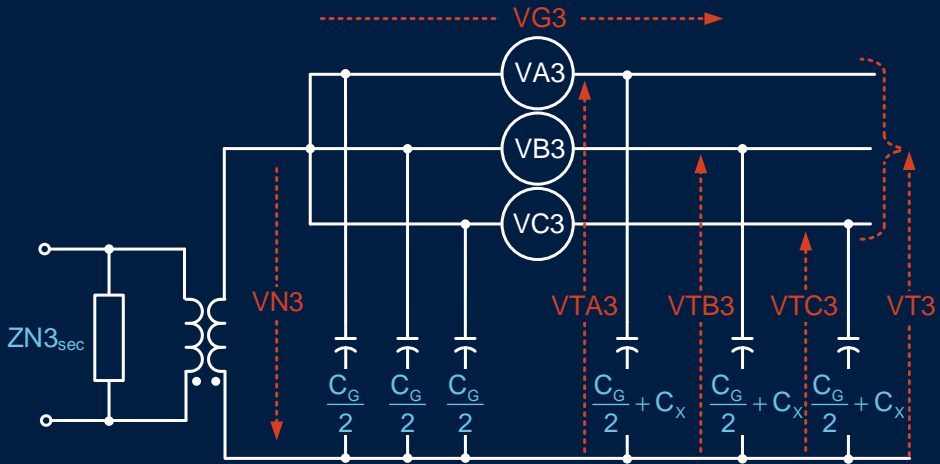


Third-Harmonic Circuit Ground Fault

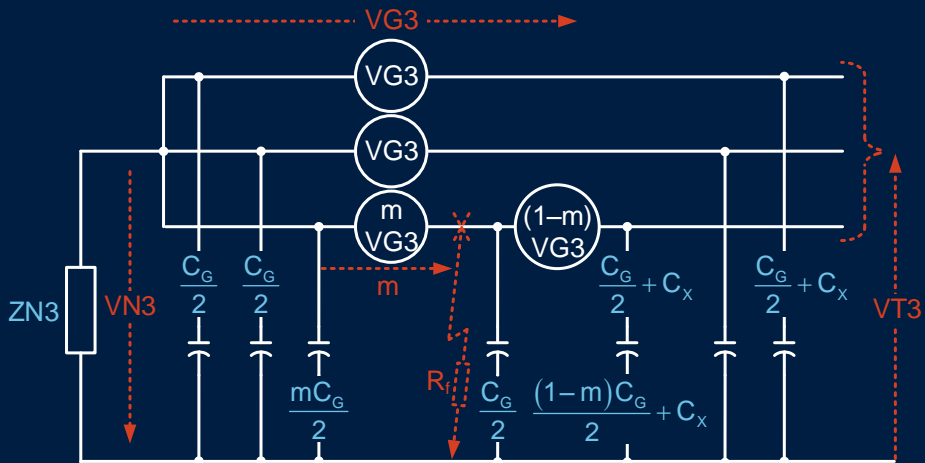

Scheme A


$$\text{Scheme A} = \frac{|VN3|}{|VN3 + VT3|} < \text{PKPA}$$

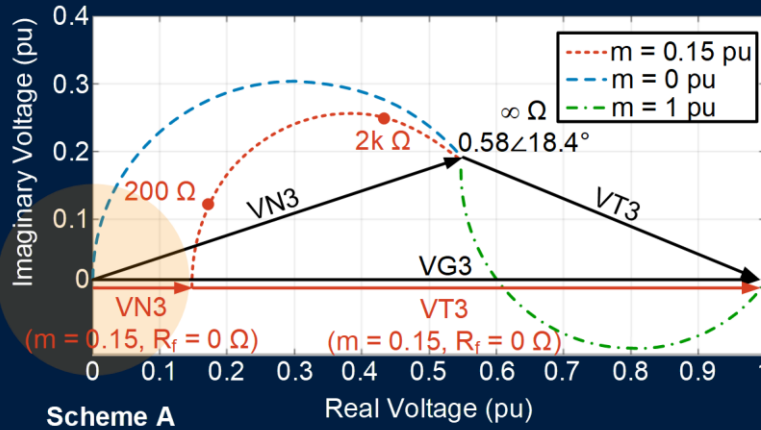

Scheme A


Scheme B

$$\text{Scheme B} = |\text{RAT} \cdot |VT3| - |VN3|| > \text{PKPB}$$

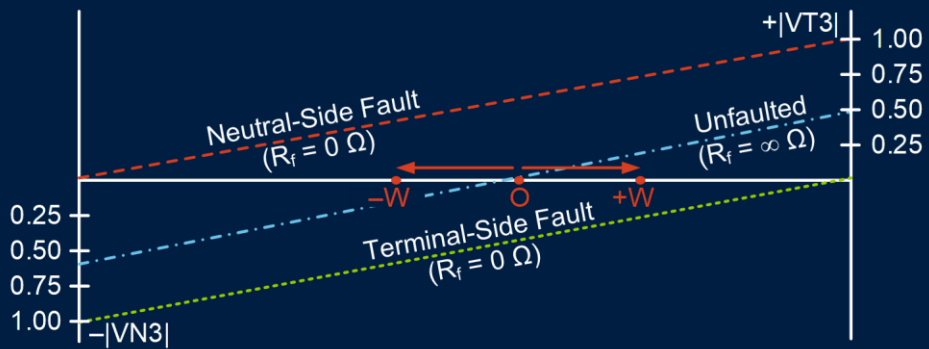

Schemes B, C, and D


$$\text{Scheme B} = |\text{RAT} \cdot |\text{VT3}| - |\text{VN3}| > \text{PKPB}$$

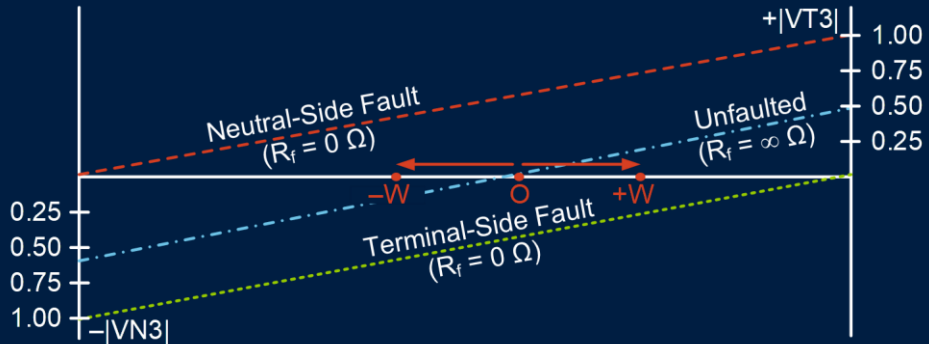



$$\text{Scheme C} = \frac{|\text{VT3}|}{|\text{VN3}|} > \text{PKPC}$$

$$\text{Scheme D} = |\text{RAT} \cdot \text{VT3} - \text{VN3}| > \text{PKPD} \cdot |\text{VN3}|$$


Security PT Secondary Faults

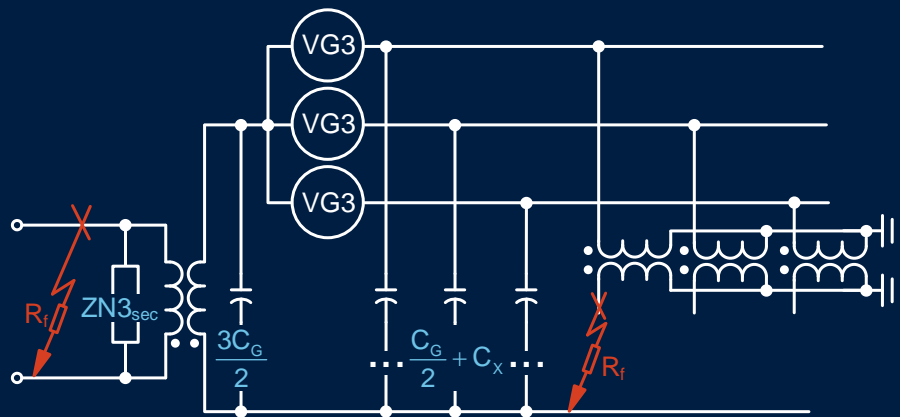

Security System Events

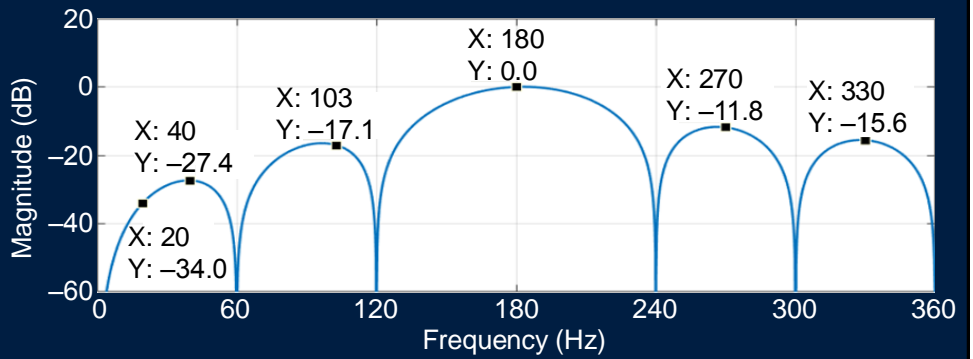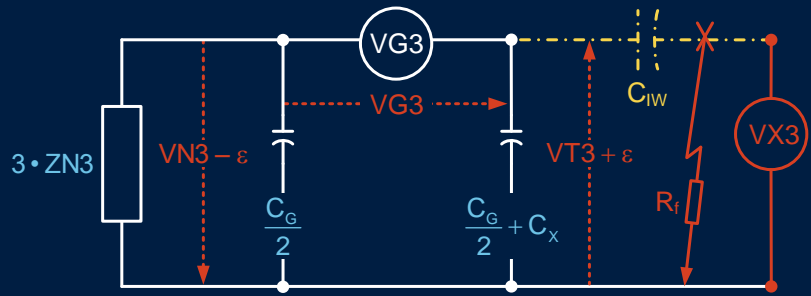


Security GSU Events

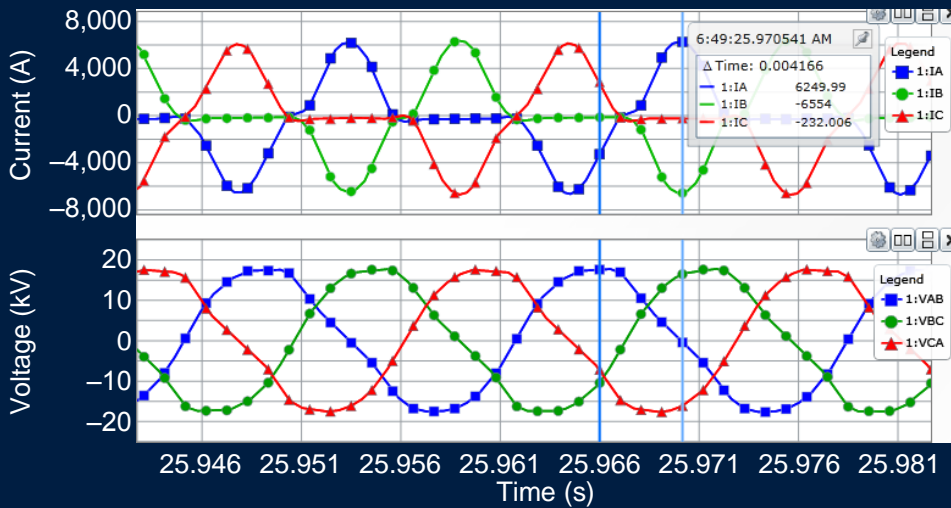


Security

Variation of Stator Ground Capacitance

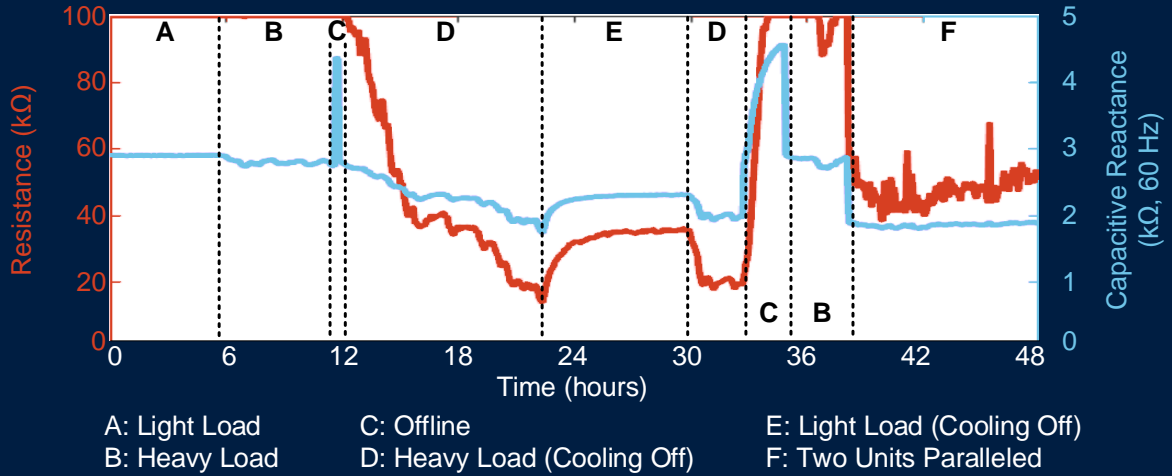

Security

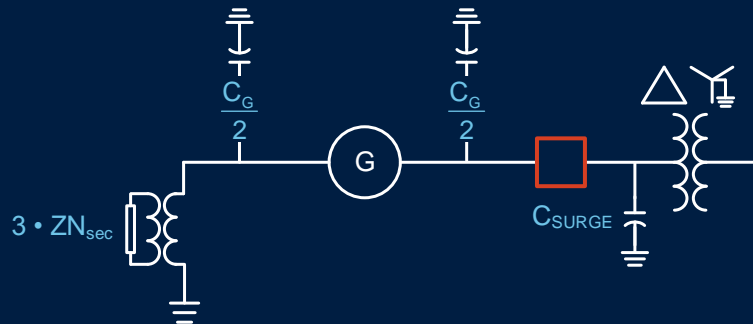
Impedance Profile Change at Generator Terminal



Security Settings


ϵ (pu of VG3)	Scheme A PKP	Scheme B PKP	Scheme C PKP	Scheme D PKP
0.00	0.58	0.00	1.00	0.00
0.10	0.48	0.20	1.41	0.43
0.20	0.38	0.40	2.04	1.08
0.28	0.30	0.56	2.87	1.92
0.43	0.15	0.88	6.79	5.85

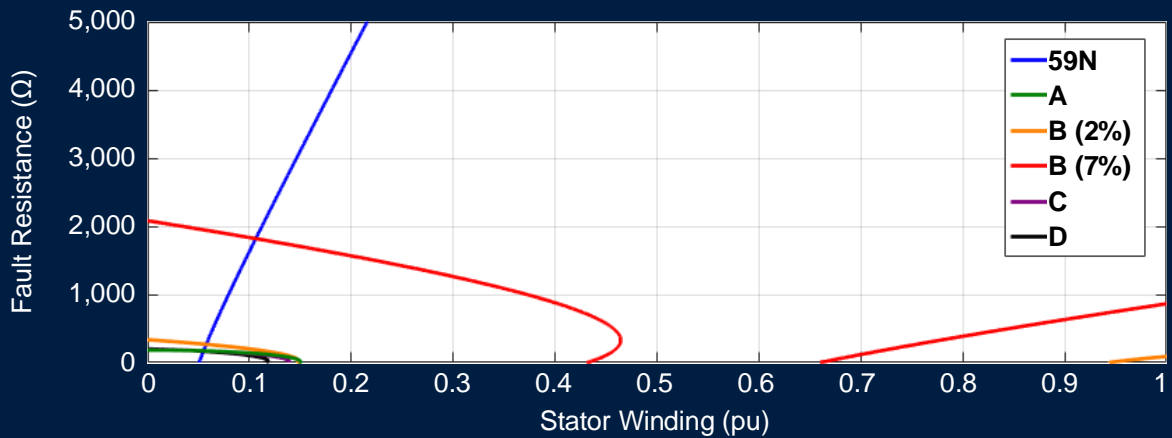Sensitivity Secure Settings ($\epsilon = 0.43$ pu)



Sensitivity

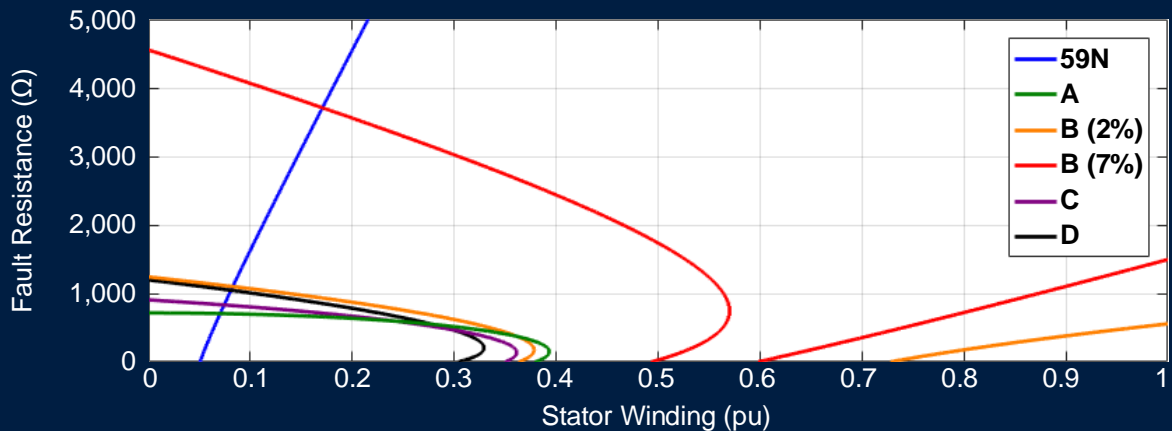Sensitive Settings ($\varepsilon = 0.20$ pu)



Conclusions

- Not all schemes are the same
- Schemes can be set with similar levels of security or sensitivity
- When set consistently, all schemes are adequate for secure tripping

Questions?

