

# Fault Currents, Circuit Breakers, and a New Method for X/R Calculations in Parallel Circuits


Amir Norouzi

*Schweitzer Engineering Laboratories, Inc.*

# Outline


- 1) Fault Currents and Circuit Breaker Rating
- 2) Fault Current Characteristics in Parallel Circuits
- 3) Transient Current Calculation: A General Approach
- 4) The Concept of a Variable  $X/R$
- 5) Conclusions
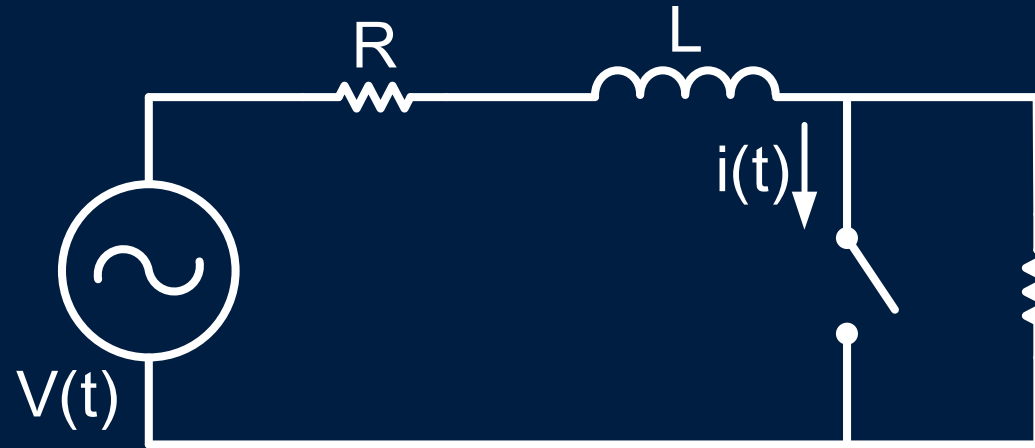
# Fault Currents and Circuit Breaker Rating



$$i(t) = \underbrace{\frac{V_m}{Z} \sin(\omega t + \theta - \alpha)}_{\text{steady state}} - \underbrace{\left[ \frac{V_m}{Z} \sin(\theta - \alpha) - i(0) \right] e^{-\frac{\omega t}{X/R}}}_{\text{transient}}$$
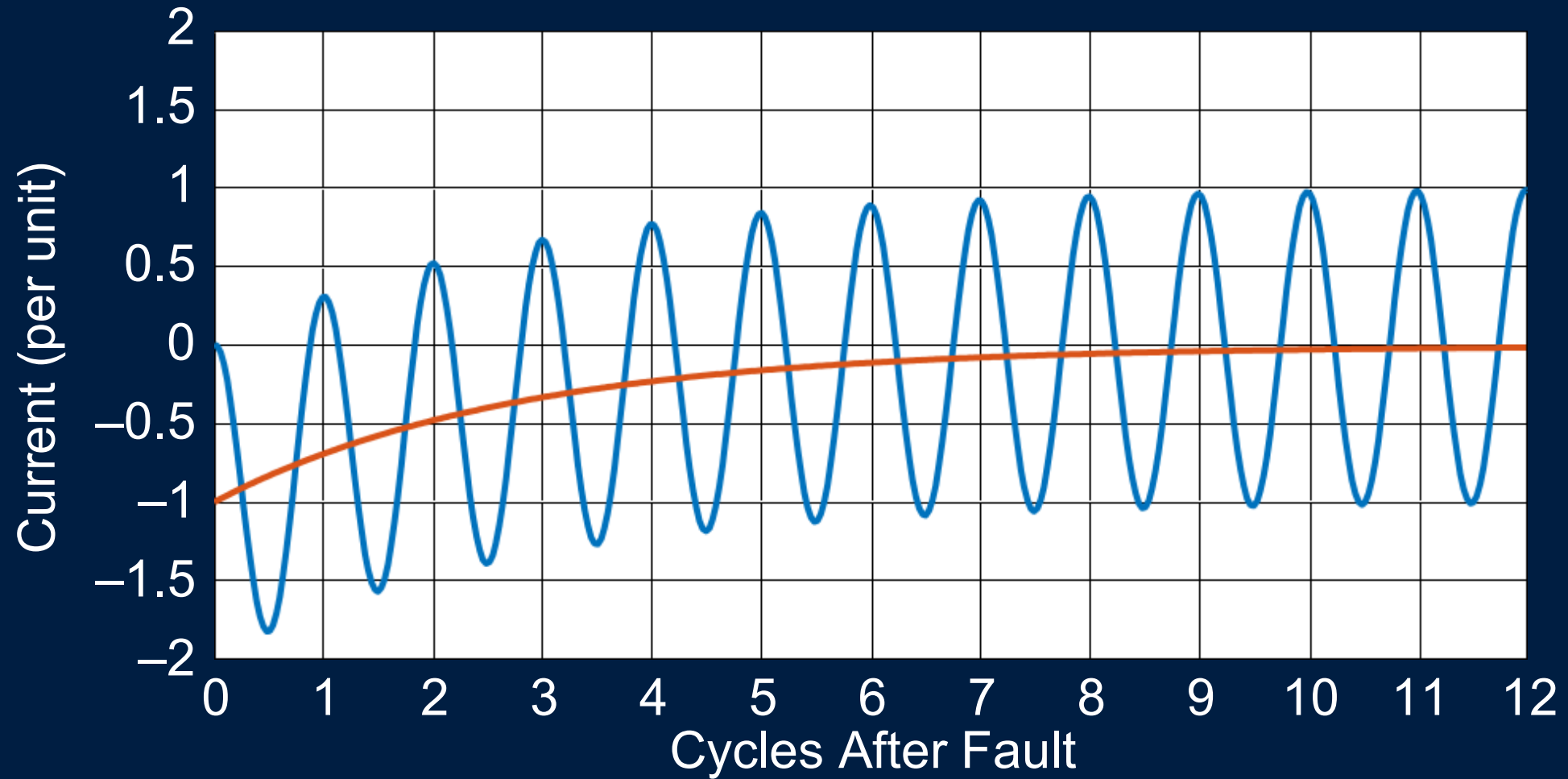
# Fault Currents and Circuit Breaker Rating



# Fault Currents and Circuit Breaker Rating


Total *rms* value of the combined ac and dc currents

$$I_{\text{asym}} = I_{\text{sym}} \sqrt{1 + 2e^{\frac{-2\omega t}{X/R}}}$$

Symmetrical-based rating

$$I_{\text{sym}} \text{ and } \frac{X}{R} = 17$$
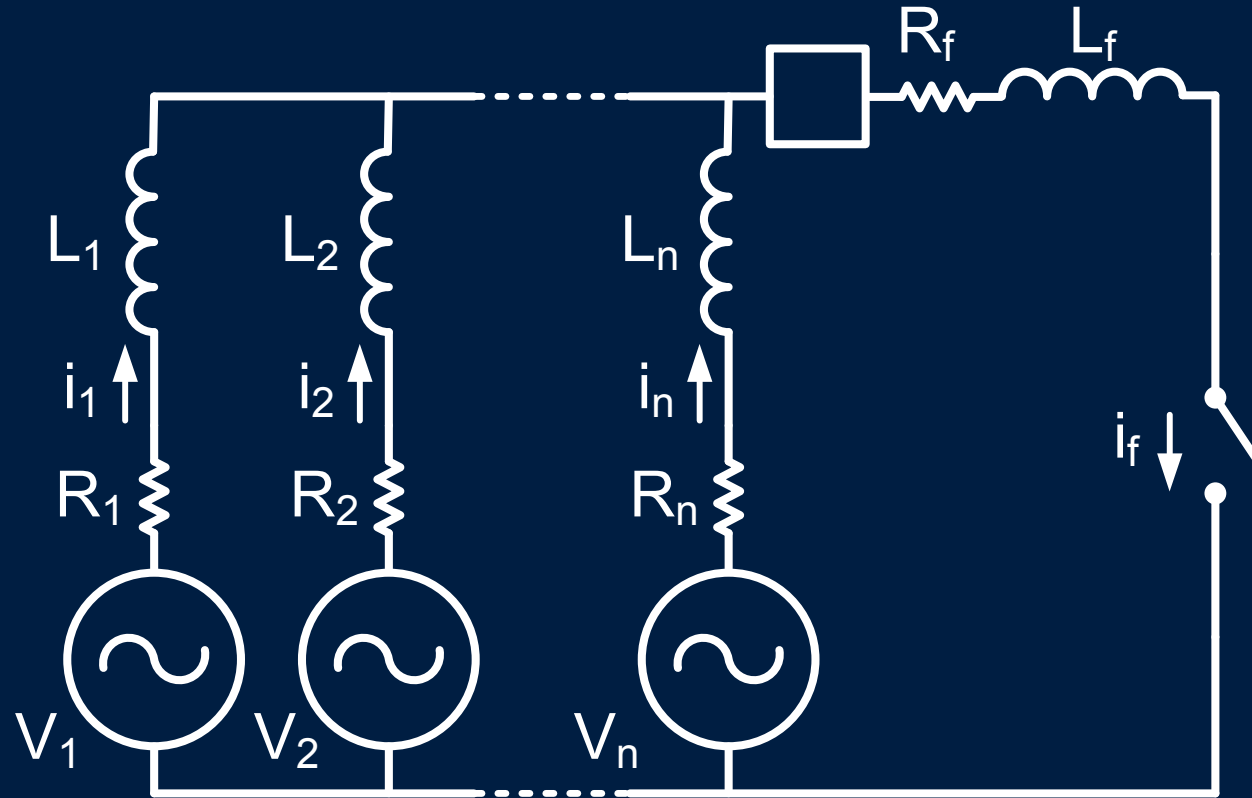
# Fault Current Characteristics in Parallel Circuits



- Transient current consists of  $n$  components
- $I_1 e^{\alpha_1 t} + I_2 e^{\alpha_2 t} \neq I e^{at} \Rightarrow$  No single  $X/R$  can be defined

# Fault Current Characteristics in Parallel Circuits

- A single X/R cannot provide accurate fault current
- Decaying sinusoidal components may exist

$$[I \cos(\beta t)] e^{\alpha t}$$

# Transient Current Calculation: A General Approach

- Phasor calculations not adequate
- Need to solve differential equation of fault current
- Direct methods need substantial computing resources



# Transient Current Calculation: A General Approach

- Power systems are linear and time-invariant
- ODE solution using algebraic operations

# Transient Current Calculation: A General Approach

## Key Steps

- 1) Direct setup of ODE without KVL or KCL


$$[I(s)] = \frac{1}{|A|} [\mathcal{F}(s)] \Rightarrow |A| \text{ will provide the ODE with a pattern}$$

- 2) Initial conditions calculations

$i_k(0^+)$  and its  $(n - 1)$  derivatives need to be calculated


# Transient Current Calculation: A General Approach

## Example 1: Third Order Circuit

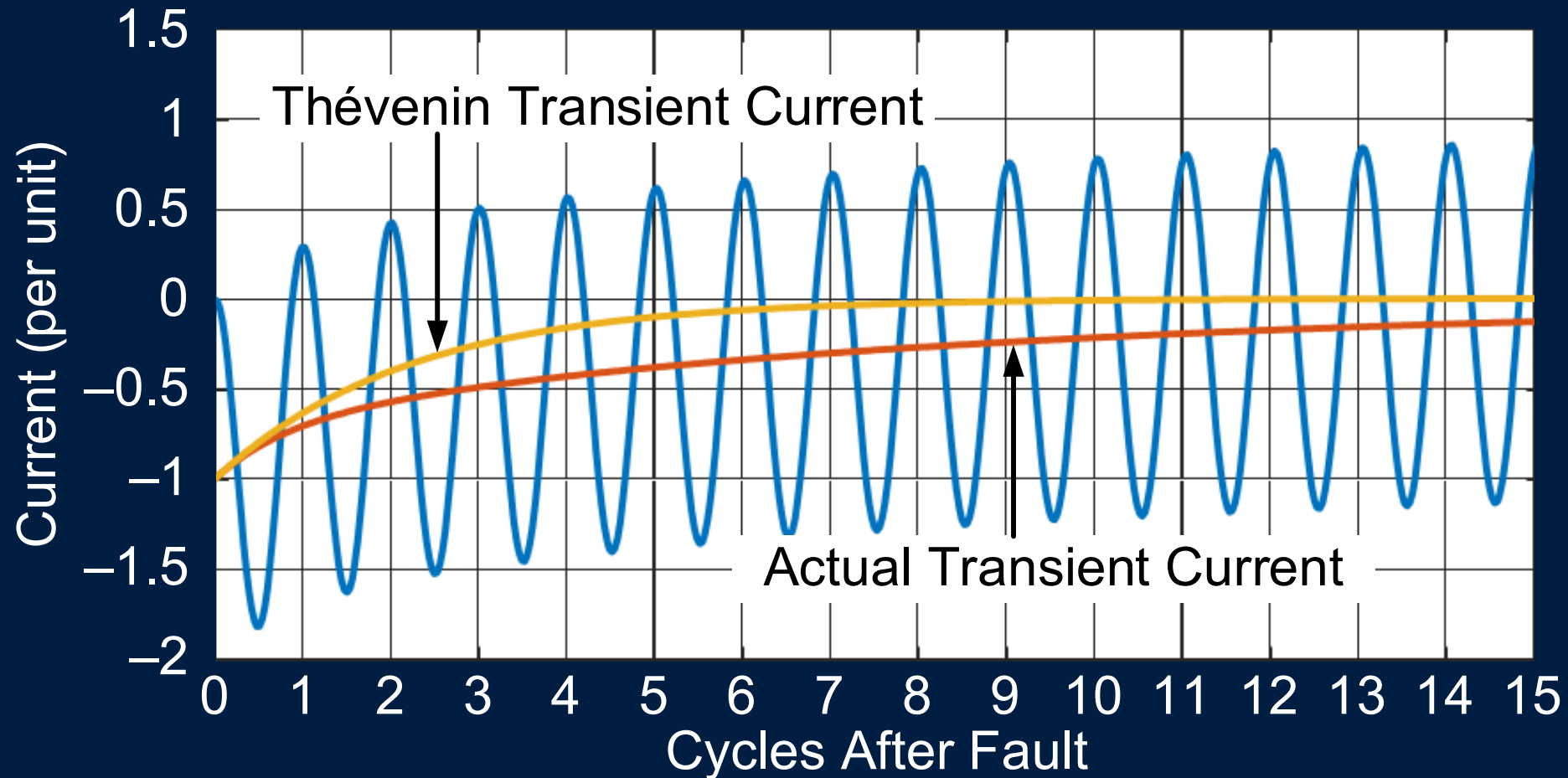

# Transient Current Calculation: A General Approach

## Example 2: Fourth Order Circuit

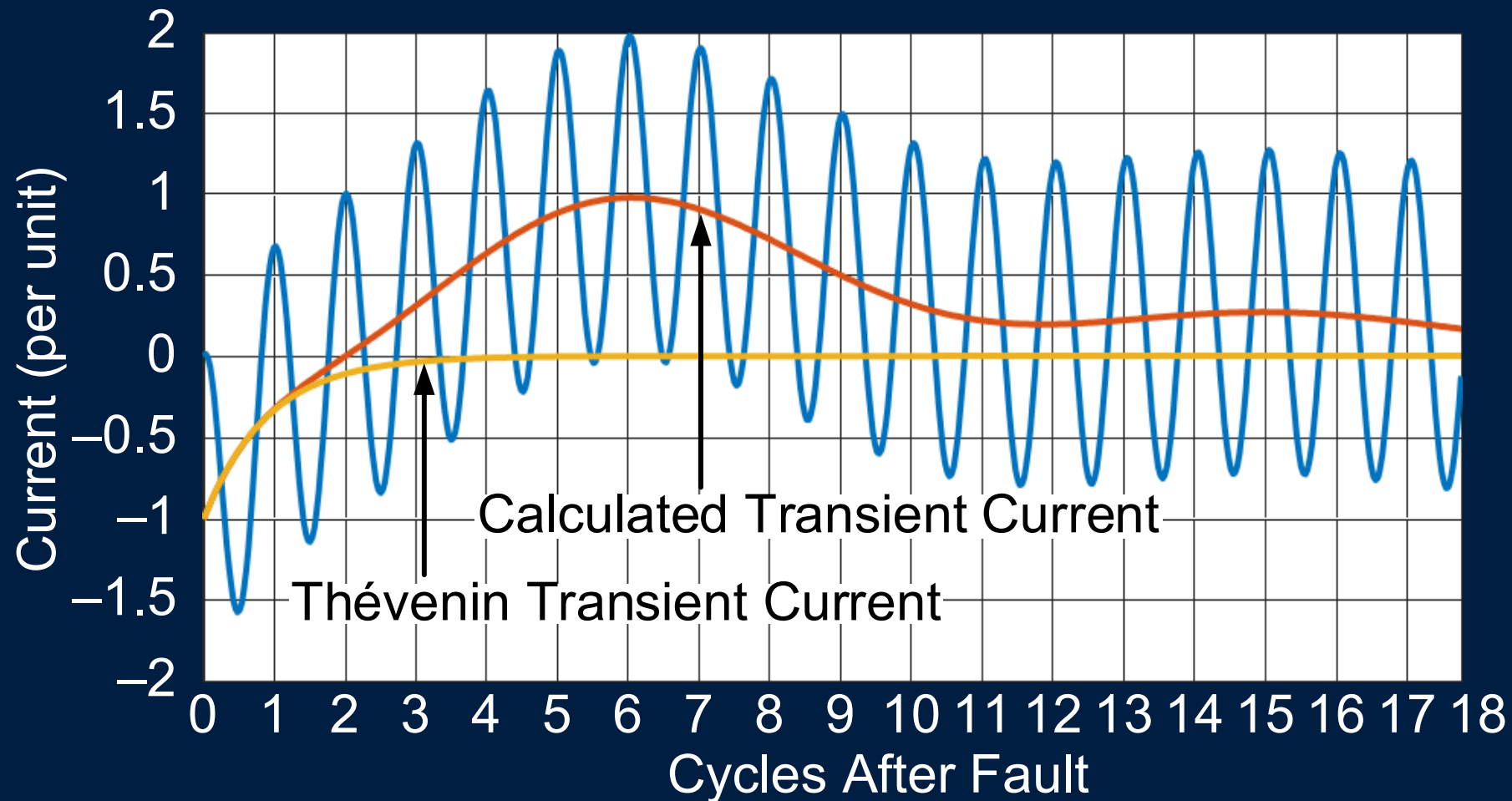


# The Concept of a Variable X/R

## RMS Value of Combined AC and DC Currents

$$I_{\text{asym}} = \sqrt{I_{\text{sym}}^2 + I_{\text{tr.}}^2}$$


# The Concept of a Variable X/R

## Total RMS Current of Example 1

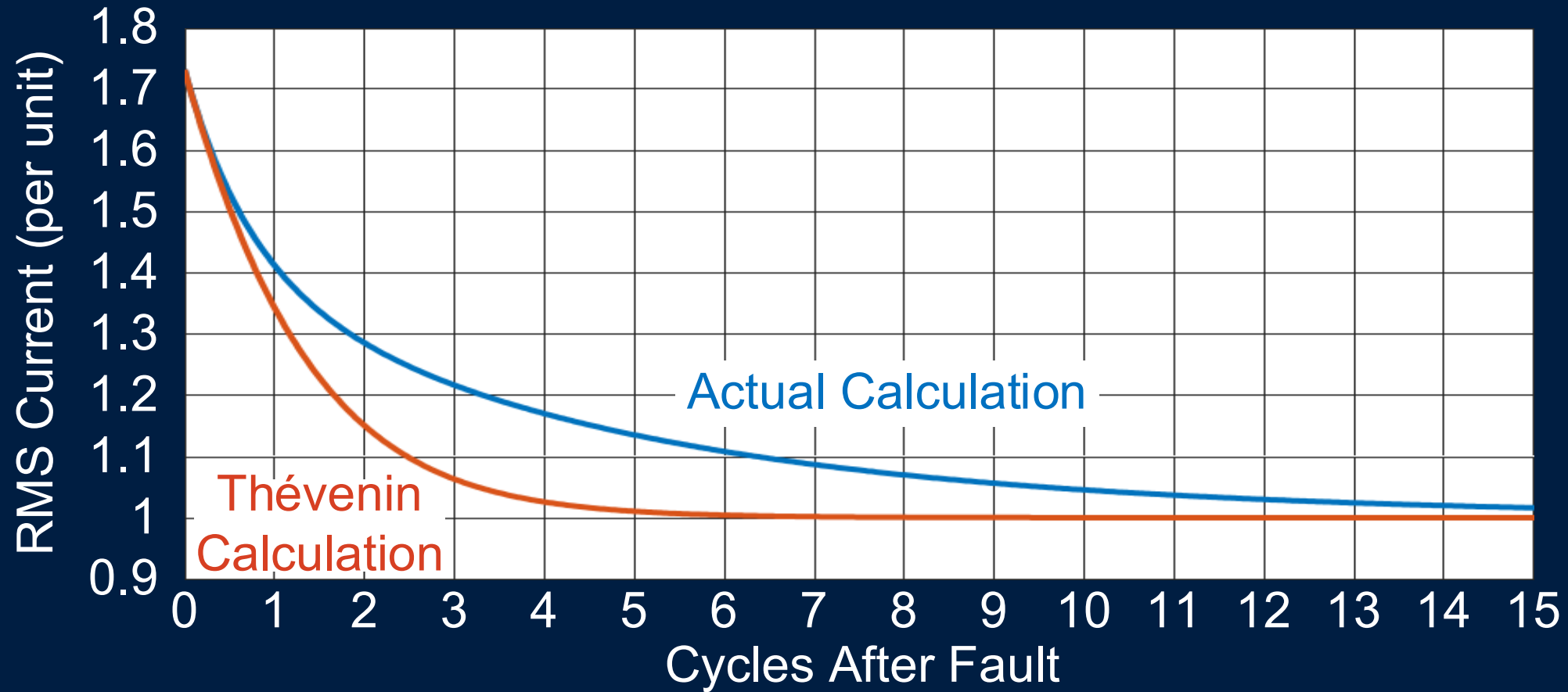

# The Concept of a Variable X/R

## Total RMS Current of Example 2

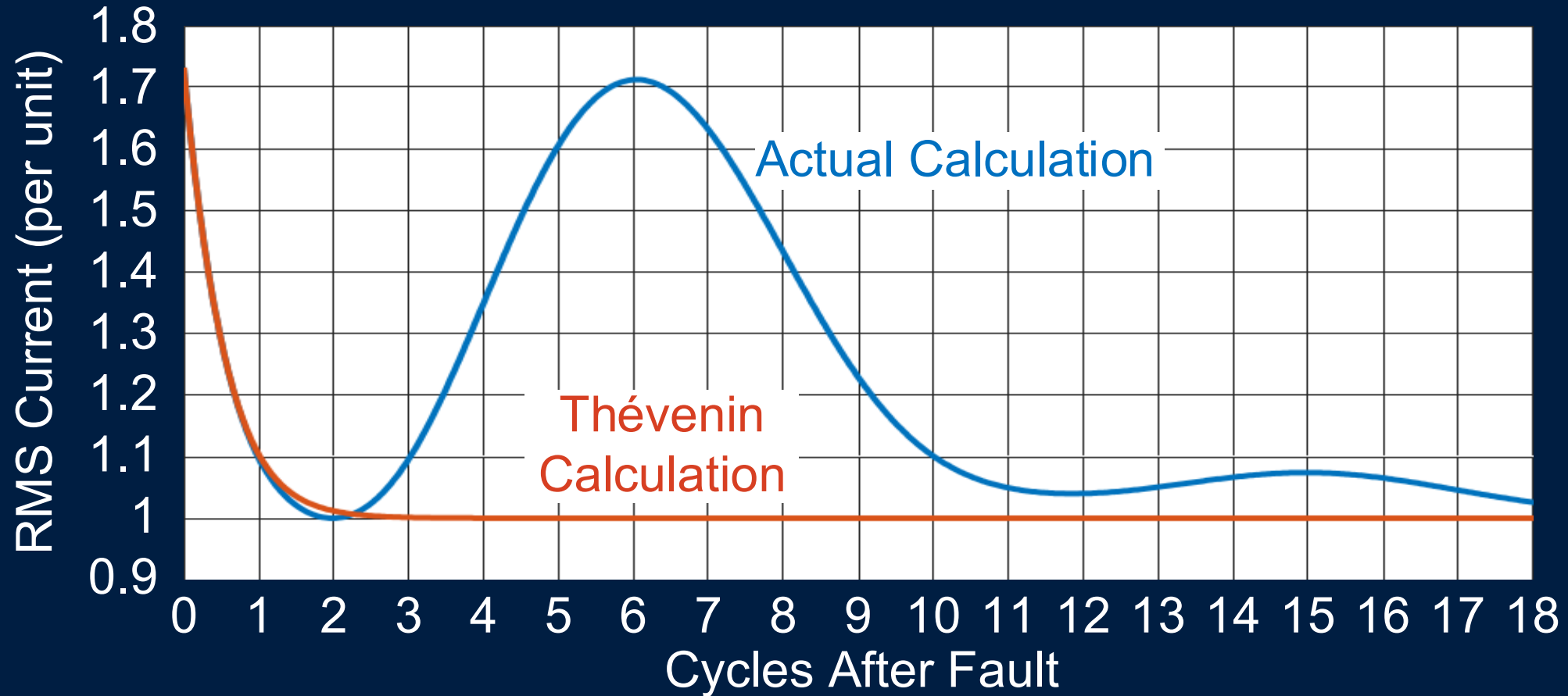

# The Concept of a Variable X/R

## Basic Concept


- 1) Calculate the accurate total *rms* current ( $I_{\text{asym}}$ )
- 2) Calculate a time-varying X/R from  $I_{\text{asym}}$  and  $I_{\text{sym}}$

$$I_{\text{asym}} = I_{\text{sym}} \sqrt{1 + 2e^{\frac{-2\omega t}{X/R}}}$$



# The Concept of a Variable X/R

## Variable X/R in Example 1

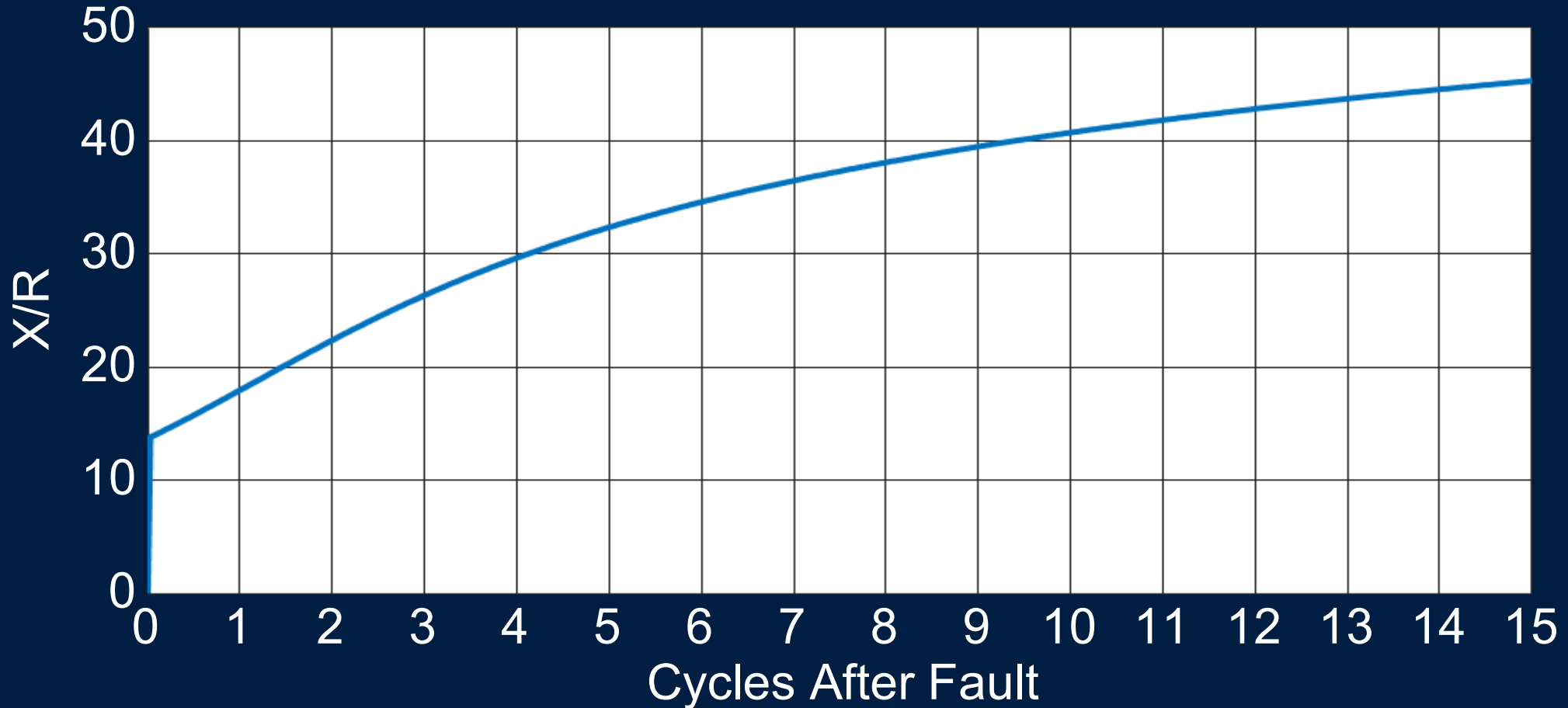

# Conclusions

- A single  $X/R$  not an accurate description of fault current
- Fault's ODE can be algebraically set up and solved
- A variable  $X/R$  links rating standards with actual current

**Questions?**