

**TEXAS A&M  
UNIVERSITY**

MARCH 28-31, 2022

75th Annual

# **Conference for Protective Relay Engineers**

## Application of Standard Three Phase Power Transformer Protection Relays to Special Railway Transformers

Mike Kockott, Zoran Gajić, Bharadwaj Vasudevan, Alexandre Piatniczka

# Overview

---

- Introduction
- 87T protection for
  - Three-phase, two-winding power transformer
  - Three-phase, three-winding power transformer
  - Single-phase railway transformer
  - Split single-phase railway transformer
  - Railway autotransformer
  - Scott transformer
- Other protections
- Conclusions

# Introduction

---

- Triggered by a US project
- Objective: to show how to use standard three-phase transformer protection relays to protect 50/60Hz railway transformers
  - 50/60Hz railway systems are found in many countries around the world, including the US
- To bear in mind:
  - three-phase transformer protection relays treat the analog quantities in a three-phase manner
  - for non three-phase railway transformer applications the analog quantities will be treated in the same way

# Three-phase, two-winding power transformer

- Balanced through-load


$$\begin{aligned} |I_{W1}| &= \frac{V_{W2}}{V_{W1}} * |I_{W2}| \\ &= \frac{V_{LV}}{V_{HV}} * |I_{W2}| \end{aligned}$$

- Per phase differential currents for Dd0 transformer

$$\overline{ID\_A} = \overline{IA_{HV}} + \frac{V_{LV}}{V_{HV}} * \overline{IA_{LV}}$$

$$\overline{ID\_B} = \overline{IB_{HV}} + \frac{V_{LV}}{V_{HV}} * \overline{IB_{LV}}$$
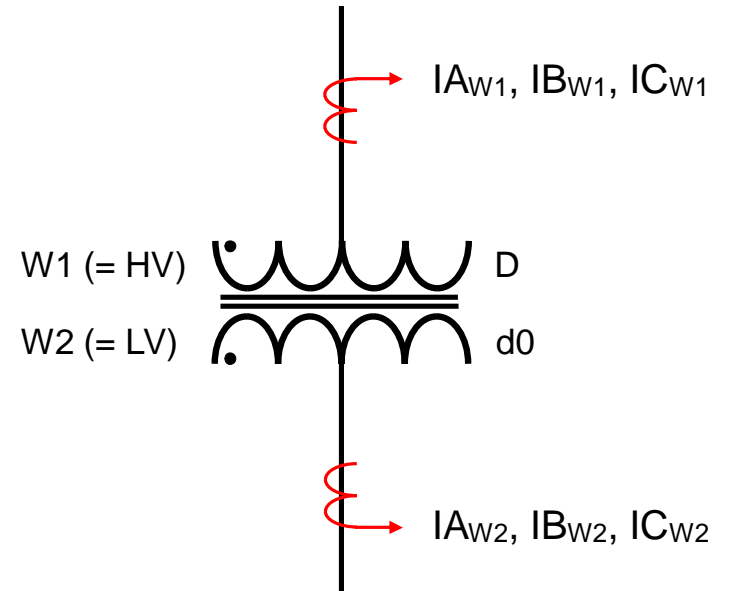
$$\overline{ID\_C} = \overline{IC_{HV}} + \frac{V_{LV}}{V_{HV}} * \overline{IC_{LV}}$$




# Three-phase, two-winding power transformer

- Differential current matrix equation for Dd0 transformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IA_{HV}} \\ \overline{IB_{HV}} \\ \overline{IC_{HV}} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IA_{LV}} \\ \overline{IB_{LV}} \\ \overline{IC_{LV}} \end{bmatrix}$$
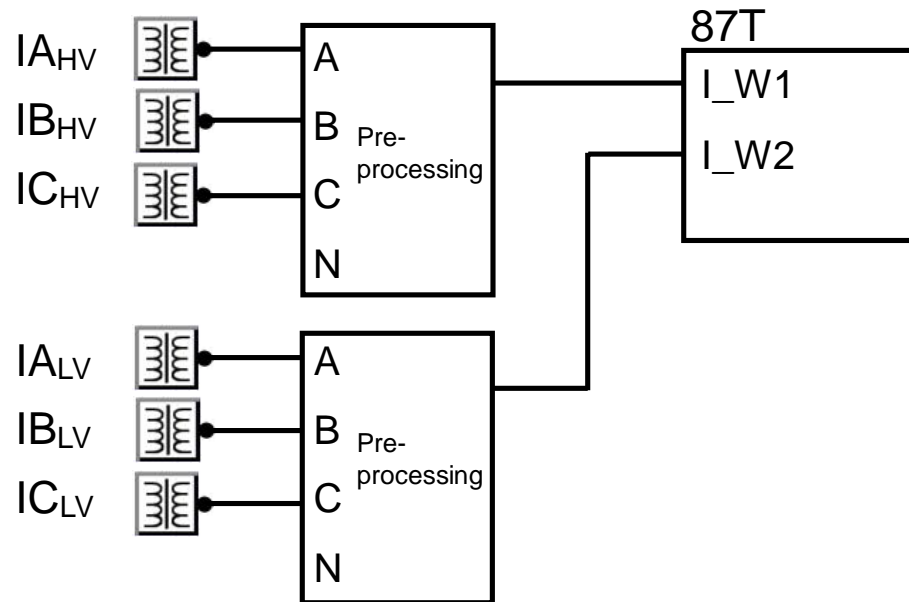
# Three-phase, two-winding power transformer

- Connection of currents to the 87T function



# Three-phase, two-winding power transformer

- Rated values

W1	$S_{R1} = S$	$V_{R1} = V_{HV}$	$I_{R1} = \frac{S}{\sqrt{3} \cdot V_{HV}}$
W2	$S_{R2} = S$	$V_{R2} = V_{LV}$	$I_{R2} = \frac{S}{\sqrt{3} \cdot V_{LV}}$

- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Clock Number W2	0 (0 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off

# Three-phase, two-winding power transformer

- Example

Dd0 transformer       $S = 120\text{MVA}$        $V_{R1} = 230\text{kV}$        $V_{R2} = 66\text{kV}$

For balanced through-load, for LV-side currents = 524.9A = 50% $I_{R2}$ , HV-side currents will be = 150.6A

$$I_{A_{HV}} = 150.6\angle 0^\circ \qquad I_{A_{LV}} = 524.9\angle 180^\circ$$

$$I_{B_{HV}} = 150.6\angle -120^\circ \qquad I_{B_{LV}} = 524.9\angle 60^\circ$$

$$I_{C_{HV}} = 150.6\angle 120^\circ \qquad I_{C_{LV}} = 524.9\angle -60^\circ$$

$$\begin{aligned} \begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} &= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 150.6\angle 0^\circ \\ 150.6\angle -120^\circ \\ 150.6\angle 120^\circ \end{bmatrix} + \frac{66}{230} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 524.9\angle 180^\circ \\ 524.9\angle 60^\circ \\ 524.9\angle -60^\circ \end{bmatrix} \\ &= \begin{bmatrix} 150.6\angle 0^\circ \\ 150.6\angle -120^\circ \\ 150.6\angle 120^\circ \end{bmatrix} + \begin{bmatrix} 150.6\angle 180^\circ \\ 150.6\angle 60^\circ \\ 150.6\angle -60^\circ \end{bmatrix} \end{aligned}$$




# Three-phase, three-winding power transformer

- Differential current matrix equation for Dd0d0 transformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{matrix} \text{I\_W1} \\ \begin{bmatrix} \overline{IA_{HV}} \\ \overline{IB_{HV}} \\ \overline{IC_{HV}} \end{bmatrix} \end{matrix} + \frac{V_{MV}}{V_{HV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{matrix} \text{I\_W2} \\ \begin{bmatrix} \overline{IA_{MV}} \\ \overline{IB_{MV}} \\ \overline{IC_{MV}} \end{bmatrix} \end{matrix} \\
 + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{matrix} \text{I\_W3} \\ \begin{bmatrix} \overline{IA_{LV}} \\ \overline{IB_{LV}} \\ \overline{IC_{LV}} \end{bmatrix} \end{matrix}$$
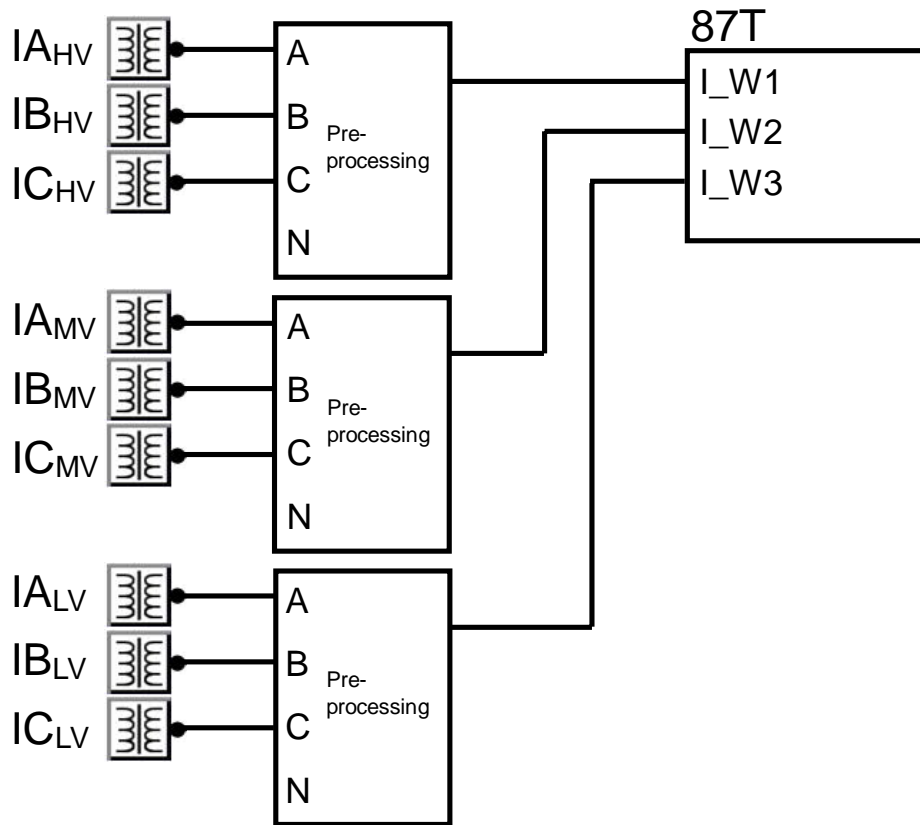
# Three-phase, three-winding power transformer

- Connection of currents to the 87T function



- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Voltage W3	$V_{R3}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Rated Current W3	$I_{R3}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Connect Type W3	Delta (D)
Clock Number W2	0 (0 deg)
Clock Number W3	0 (0 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off
ZS Current Subtraction W3	Off

# Single-phase railway transformer

- Balanced through-load

$$|IA| = \frac{V_{LV}}{V_{HV}} * |IM|$$


$$|IC| = \frac{V_{LV}}{V_{HV}} * |IN|$$

- Per phase differential currents

$$\overline{ID\_A} = \overline{IA} + \frac{V_{LV}}{V_{HV}} * \overline{IM}$$

$$\overline{ID\_B} = 0$$
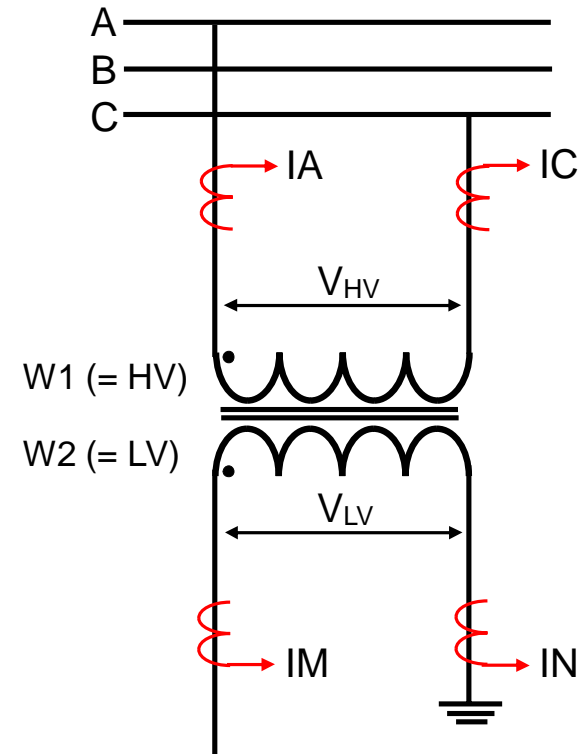
$$\overline{ID\_C} = \overline{IC} + \frac{V_{LV}}{V_{HV}} * \overline{IN}$$




# Single-phase railway transformer

- Differential current matrix equation for single-phase railway transformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IA} \\ 0 \\ \overline{IC} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IM} \\ 0 \\ \overline{IN} \end{bmatrix}$$
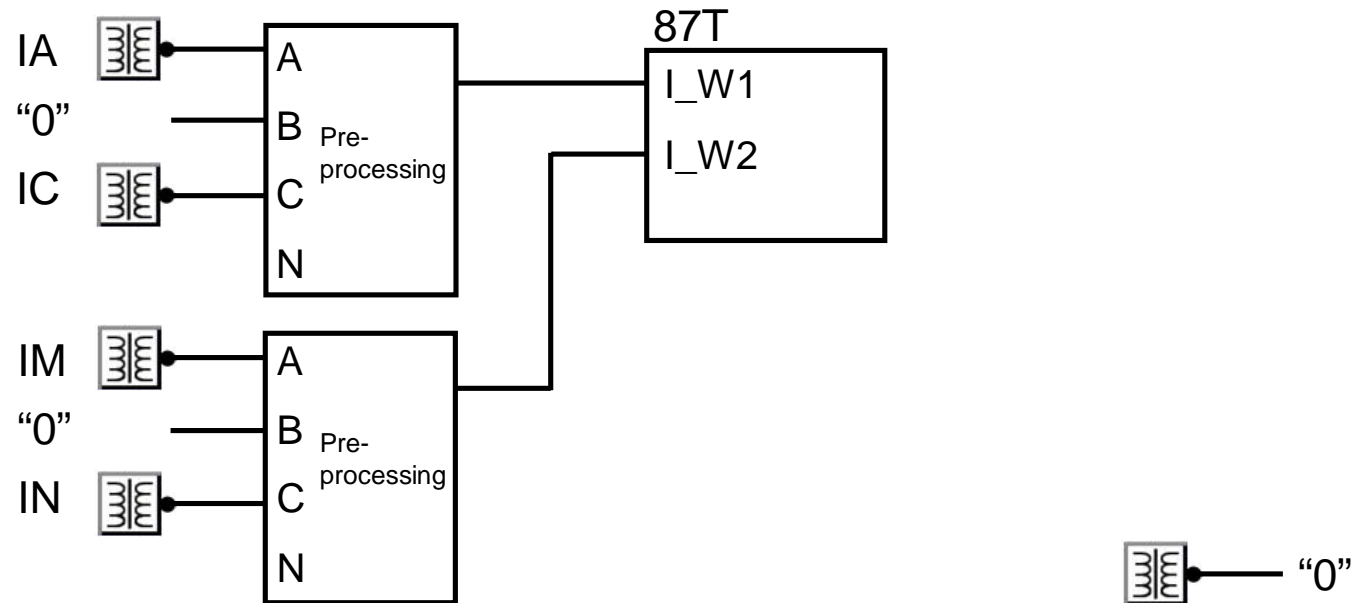
# Single-phase railway transformer

- Connection of currents to the 87T function



# Single-phase railway transformer

- Rated values

W1	$S_{R1} = S$	$V_{R1} = V_{HV}$	$I_{R1} = \frac{S}{V_{HV}}$
W2	$S_{R2} = S$	$V_{R2} = V_{LV}$	$I_{R2} = \frac{S}{V_{HV}}$

- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Clock Number W2	0 (0 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off

# Single-phase railway transformer


- Example

Single-phase railway transformer       $S = 30\text{MVA}$        $V_{R1} = 115\text{kV}$        $V_{R2} = 27.5\text{kV}$

For balanced through-load, for LV-side currents =  $545.4\text{A} = 50\%I_{R2}$ , HV-side currents will be =  $130.4\text{A}$

$$I_A = 130.4\angle 0^\circ \qquad I_M = 545.4\angle 180^\circ$$
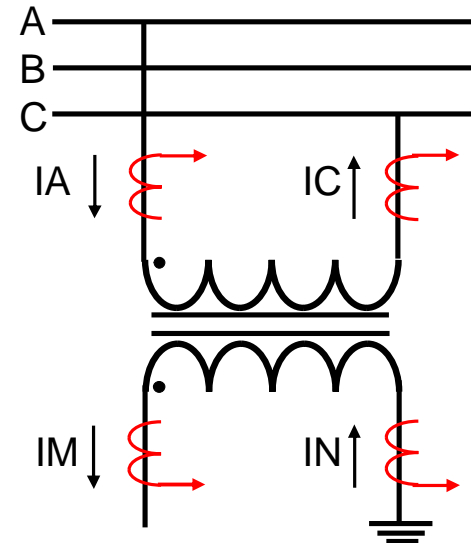
$$I_C = 130.4\angle 180^\circ \qquad I_N = 545.4\angle 0^\circ$$



# Single-phase railway transformer

- Example

Single-phase railway transformer       $S = 30\text{MVA}$        $V_{R1} = 115\text{kV}$        $V_{R2} = 27.5\text{kV}$

For balanced through-load, for LV-side currents =  $545.4\text{A} = 50\%I_{R2}$ , HV-side currents will be =  $130.4\text{A}$

$$I_A = 130.4\angle 0^\circ \qquad I_M = 545.4\angle 180^\circ$$

$$I_C = 130.4\angle 180^\circ \qquad I_N = 545.4\angle 0^\circ$$

$$\begin{bmatrix} \overline{I_{D\_A}} \\ \overline{I_{D\_B}} \\ \overline{I_{D\_C}} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 130.4\angle 0^\circ \\ 0 \\ 130.4\angle 180^\circ \end{bmatrix} + \frac{27.5}{115} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 545.4\angle 180^\circ \\ 0 \\ 545.4\angle 0^\circ \end{bmatrix}$$

$$= \begin{bmatrix} 130.4\angle 0^\circ \\ 0 \\ 130.4\angle 180^\circ \end{bmatrix} + \begin{bmatrix} 130.4\angle 180^\circ \\ 0 \\ 130.4\angle 0^\circ \end{bmatrix}$$



# Split single-phase railway transformer

- Balanced load

$$|I_A| = \frac{V_{LV}}{V_{HV}} * |I_M| + \frac{V_{LV}}{V_{HV}} * |I_S|$$


$$|I_C| = \frac{V_{LV}}{V_{HV}} * |I_S| + \frac{V_{LV}}{V_{HV}} * |I_M|$$

- Per phase differential currents

$$\overline{I_{D\_A}} = \overline{I_A} + \frac{V_{LV}}{V_{HV}} * \overline{I_M} + \frac{V_{LV}}{V_{HV}} * (-\overline{I_S})$$


$$\overline{I_{D\_B}} = 0$$
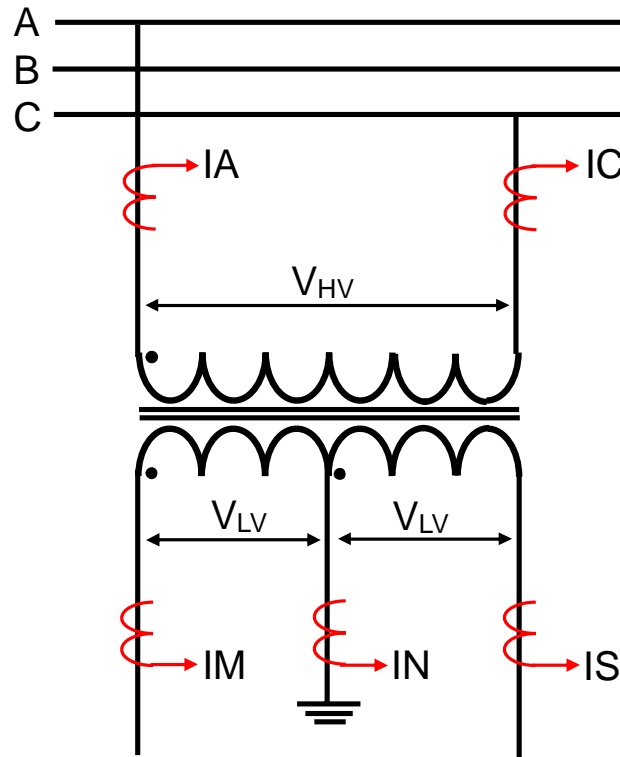
$$\overline{I_{D\_C}} = \overline{I_C} + \frac{V_{LV}}{V_{HV}} * \overline{I_S} + \frac{V_{LV}}{V_{HV}} * (-\overline{I_M})$$



$$V_{W1} = V_{HV}$$

$$V_{W2} = V_{W3} = V_{LV}$$

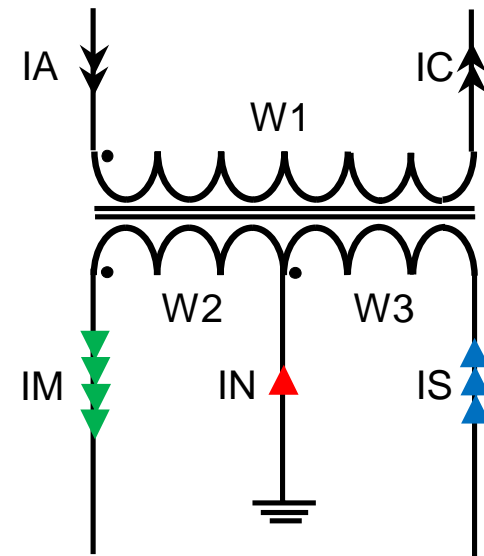



# Split single-phase railway transformer

- Differential current matrix equation for split single-phase railway transformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IA} \\ 0 \\ \overline{IC} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IM} \\ 0 \\ \overline{IS} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} \overline{IS} \\ 0 \\ \overline{IM} \end{bmatrix}$$
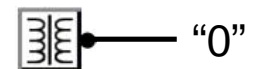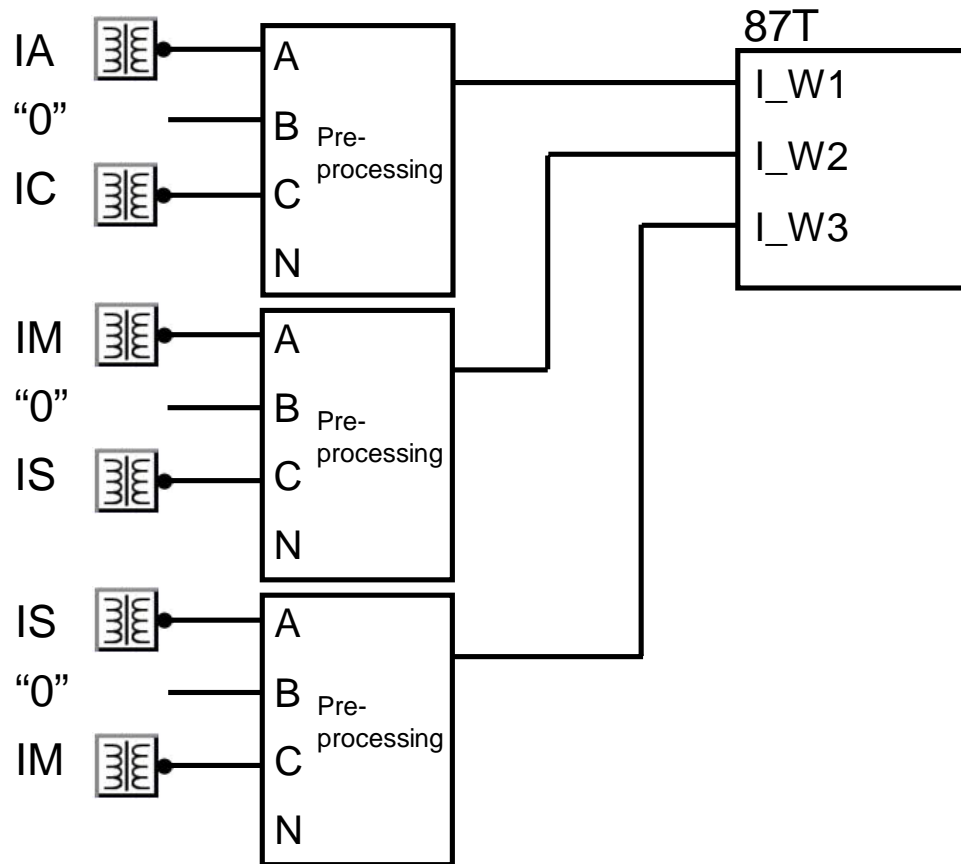
# Split single-phase railway transformer

- Connection of currents to the 87T function



# Split single-phase railway transformer

- Rated values

W1	$S_{R1} = S$	$V_{R1} = V_{HV}$	$I_{R1} = \frac{S}{V_{HV}}$
W2	$S_{R2} = \frac{S}{2}$	$V_{R2} = V_{LV}$	$I_{R2} = \frac{S}{2 \cdot V_{HV}}$
W3	$S_{R3} = \frac{S}{2}$	$V_{R3} = V_{LV}$	$I_{R3} = \frac{S}{2 \cdot V_{HV}}$

- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Voltage W3	$V_{R3}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Rated Current W3	$I_{R3}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Connect Type W3	Delta (D)
Clock Number W2	0 (0 deg)
Clock Number W3	6 (180 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off
ZS Current Subtraction W3	Off

# Split single-phase railway transformer

- Example

Split single-phase railway transformer


$$S_{R1} = 60\text{MVA}$$

$$S_{R2} = S_{R3} = 30\text{MVA}$$

$$V_{R1} = 115\text{kV}$$

$$V_{R2} = V_{R3} = 27.5\text{kV}$$

Typical LV-side load profile

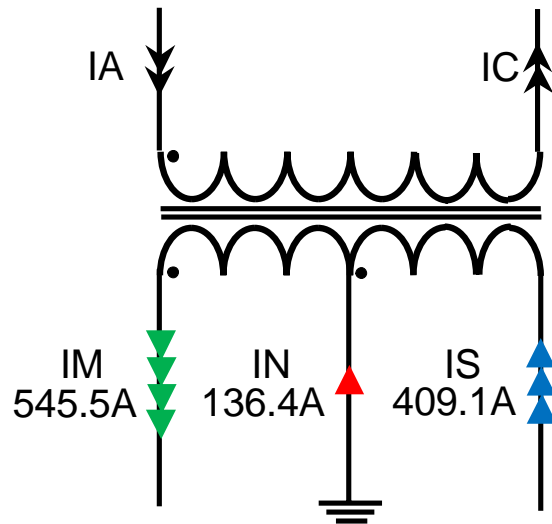

$$I_M = 545.5 \angle 180^\circ = 50\% I_{R2}$$

$$I_S = 409.1 \angle 0^\circ$$

HV-side currents for balanced load flow

$$I_A = 228.3 \angle 0^\circ$$

$$I_C = 228.3 \angle 180^\circ$$

# Split single-phase railway transformer

- Example

Split single-phase railway transformer

$$\begin{aligned}
 \begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} &= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 228.3 \angle 0^\circ \\ 0 \\ 228.3 \angle 180^\circ \end{bmatrix} + \frac{27.5}{115} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 545.4 \angle 180^\circ \\ 0 \\ 409.1 \angle 0^\circ \end{bmatrix} \\
 &+ \frac{27.5}{115} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} 409.1 \angle 0^\circ \\ 0 \\ 545.4 \angle 180^\circ \end{bmatrix} \\
 &= \begin{bmatrix} 228.3 \angle 0^\circ \\ 0 \\ 228.3 \angle 180^\circ \end{bmatrix} + \begin{bmatrix} 130.4 \angle 180^\circ \\ 0 \\ 97.8 \angle 0^\circ \end{bmatrix} + \begin{bmatrix} 97.8 \angle 180^\circ \\ 0 \\ 130.4 \angle 0^\circ \end{bmatrix}
 \end{aligned}$$

# Railway autotransformer

- Balanced load

$$|IF| = \frac{V_{LV}}{V_{HV}} * |IC|$$



$$\frac{V_{LV}}{V_{HV}} = 1$$

- Per phase differential currents

$$\overline{ID\_A} = 0$$

$$\overline{ID\_B} = 0$$
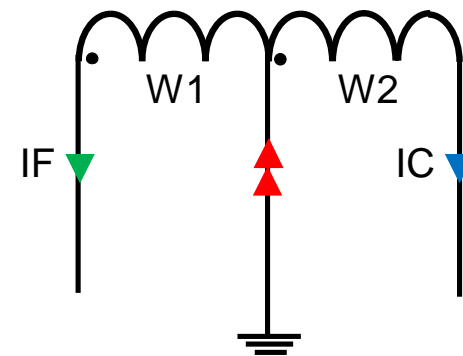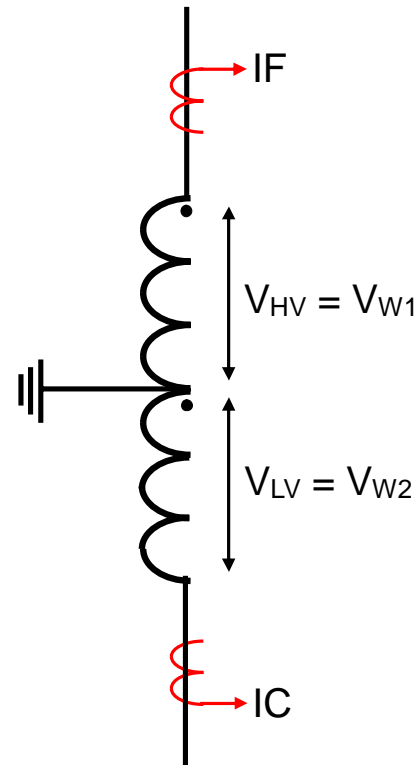
$$\overline{ID\_C} = \overline{IF} + \frac{V_{LV}}{V_{HV}} * (-\overline{IC}) = \overline{IF} + (-\overline{IC})$$



# Railway autotransformer


- Differential current matrix equation for railway autotransformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{I\_W1} \\ 0 \\ \overline{IF} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} \overline{I\_W2} \\ 0 \\ \overline{IC} \end{bmatrix}$$


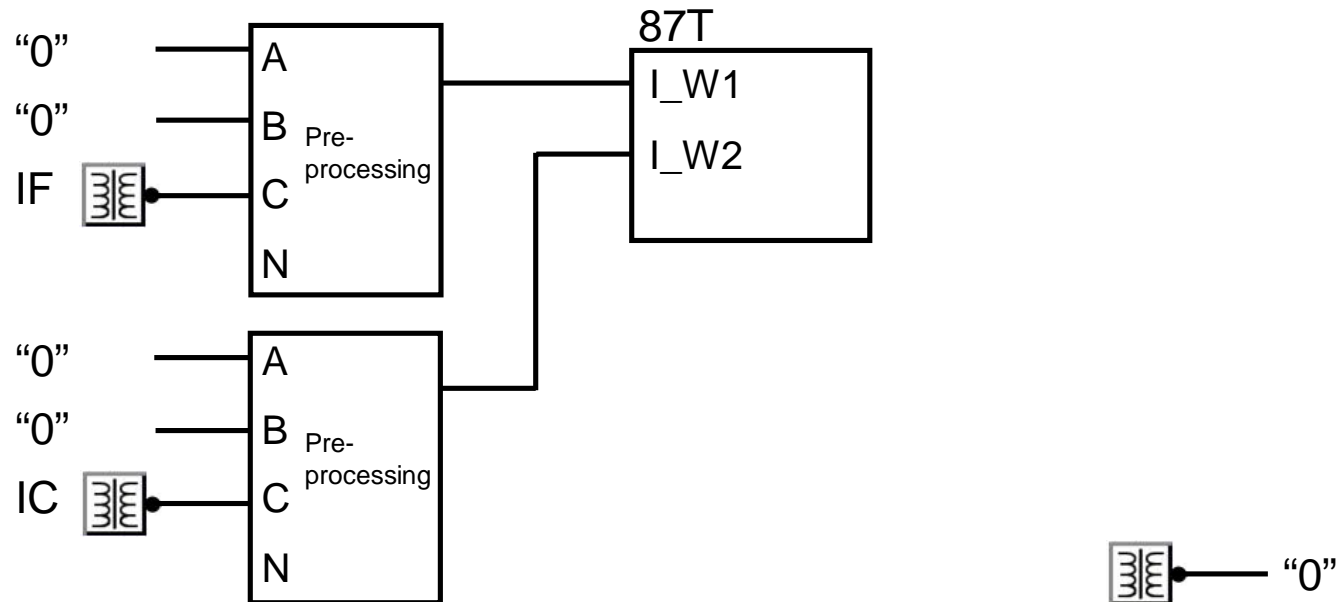
# Railway autotransformer

- Connection of currents to the 87T function



# Railway autotransformer

- Rated values

W1	$S_{R1} = S$	$V_{R1} = V_{HV} = V_{LV}$	$I_{R1} = \frac{S}{V_{HV}}$
W2	$S_{R2} = S$	$V_{R2} = V_{LV} = V_{HV}$	$I_{R2} = \frac{S}{V_{HV}}$

- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Clock Number W2	6 (180 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off

# Railway autotransformer


- Example

Railway autotransformer       $S = 5\text{MVA}$        $V_{R1} = 27.5\text{kV}$        $V_{R2} = 27.5\text{kV}$

For balanced load, for LV-side current  $I_C = 136.4\text{A}$ , HV-side  $I_F$  current will be =  $136.4\text{A}$

$$I_F = 136.4\angle 180^\circ$$

$$I_C = 136.4\angle 180^\circ$$

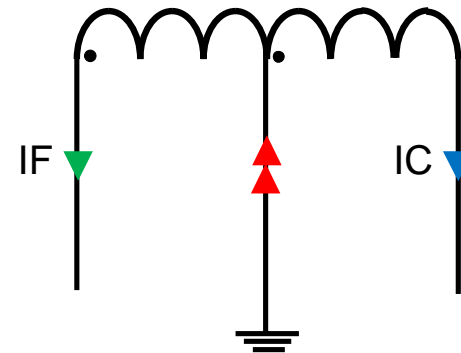

# Railway autotransformer

- Example

Railway autotransformer       $S = 5\text{MVA}$        $V_{R1} = 27.5\text{kV}$        $V_{R2} = 27.5\text{kV}$

For balanced load, for LV-side current  $I_C = 136.4\text{A}$ , HV-side IF current will be =  $136.4\text{A}$

$$I_F = 136.4\angle 180^\circ$$

$$I_C = 136.4\angle 180^\circ$$

$$\begin{bmatrix} \overline{I_{D_A}} \\ \overline{I_{D_B}} \\ \overline{I_{D_C}} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ 136.4\angle 180^\circ \end{bmatrix} + \frac{27.5}{27.5} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ 136.4\angle 180^\circ \end{bmatrix}$$

$$= \begin{bmatrix} 0 \\ 0 \\ 136.4\angle 180^\circ \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 136.4\angle 0^\circ \end{bmatrix}$$


# Railway autotransformer

- Autotransformer shared between two track sections
- Per phase differential currents

$$\overline{ID\_A} = 0$$

$$\overline{ID\_B} = 0$$
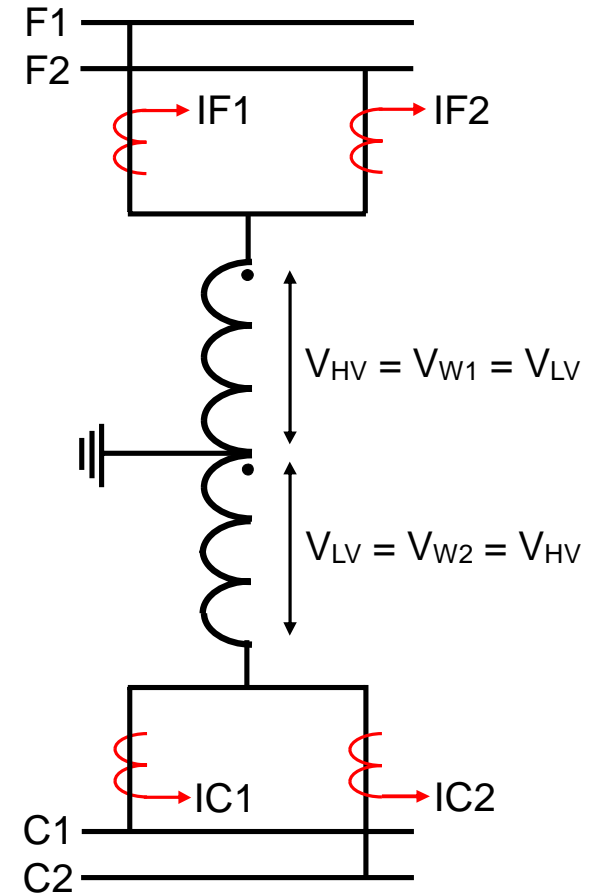
$$\begin{aligned} \overline{ID\_C} &= \overline{IF1} + \overline{IF2} + \frac{V_{LV}}{V_{HV}} * (-\overline{IC1}) + \frac{V_{LV}}{V_{HV}} * (-\overline{IC2}) \\ &= \overline{IF1} + \overline{IF2} + (-\overline{IC1} + -\overline{IC2}) \end{aligned}$$




# Railway autotransformer

- Differential current matrix equation for railway autotransformer shared between two track sections

$$\begin{aligned}
 \begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} &= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ \overline{IF1} \end{bmatrix} + \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ \overline{IF2} \end{bmatrix} \\
 &+ \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ \overline{IC1} \end{bmatrix} + \frac{V_{LV}}{V_{HV}} * \begin{bmatrix} -1 & 0 & 0 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ \overline{IC2} \end{bmatrix}
 \end{aligned}$$
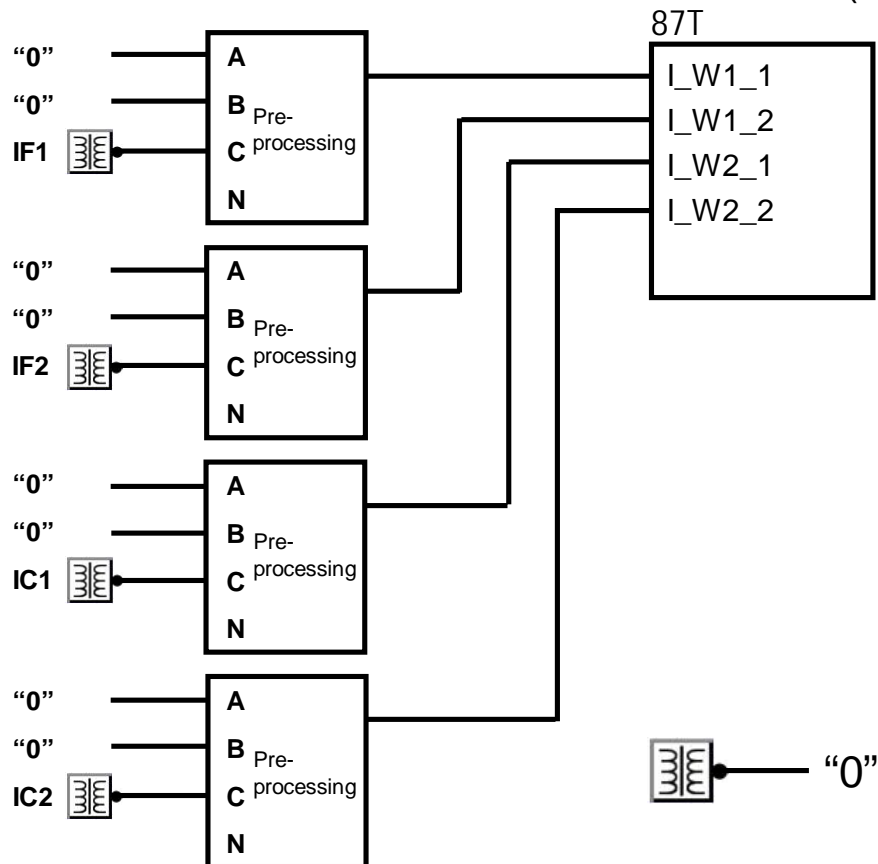
# Railway autotransformer

- Connection of currents to the 87T function (autotransformer shared between two track sections)



- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Clock Number W2	6 (180 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off

# Scott transformer

- Balanced load

$$|IM| = \frac{1/2 * V_{HV}}{V_{LV}} * |IB - IC|$$


$$|IT| = \frac{\sqrt{3} * V_{HV}}{V_{LV}} * |IA|$$

- Per phase differential currents

$$\overline{ID\_A} = \overline{IT} + \frac{\sqrt{3} * V_{HV}}{V_{LV}} * \overline{IA}$$

$$\overline{ID\_B} = 0$$
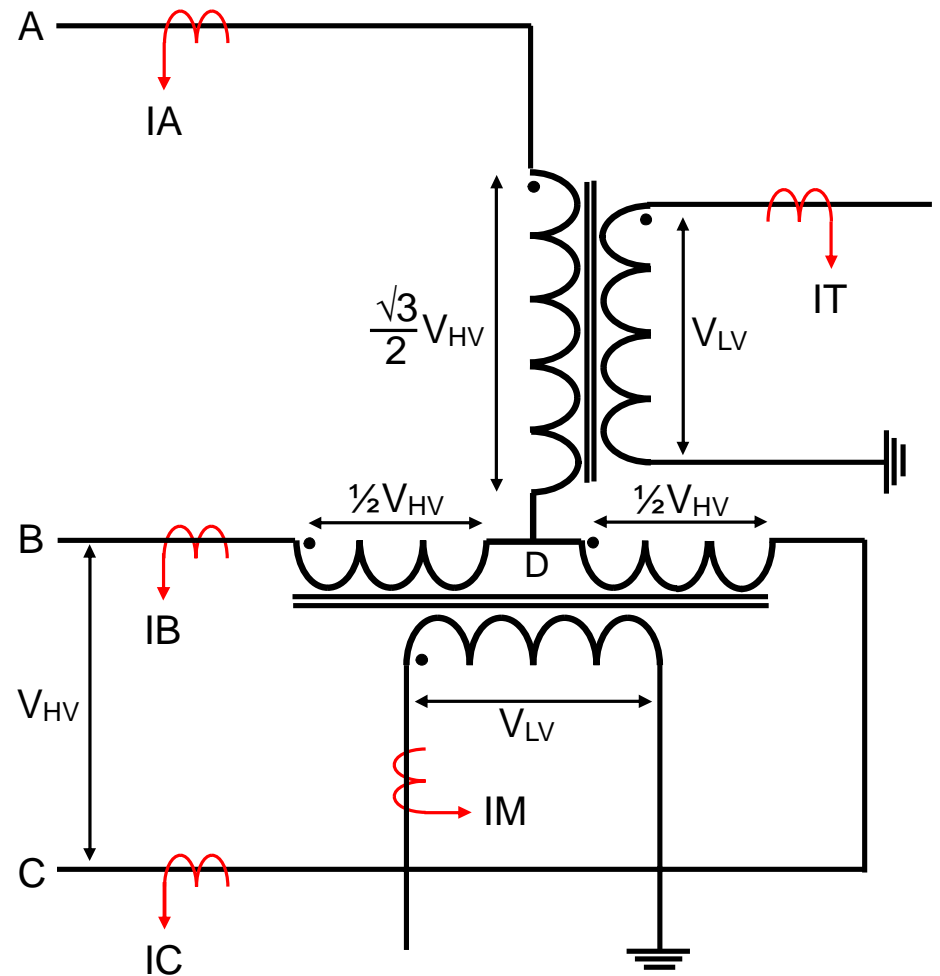
$$\overline{ID\_C} = \overline{IM} + \frac{1/2 * V_{HV}}{V_{LV}} * (\overline{IB} - \overline{IC})$$






# Scott transformer

- Differential current matrix equation for split single-phase railway transformer

$$\begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IT} \\ 0 \\ \overline{IM} \end{bmatrix} + \frac{\frac{\sqrt{3}}{2} * V_{HV}}{V_{LV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} \overline{IA} \\ 0 \\ 0 \end{bmatrix} + \frac{\frac{1}{2} * V_{HV}}{V_{LV}} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ \overline{IB - IC} \end{bmatrix}$$
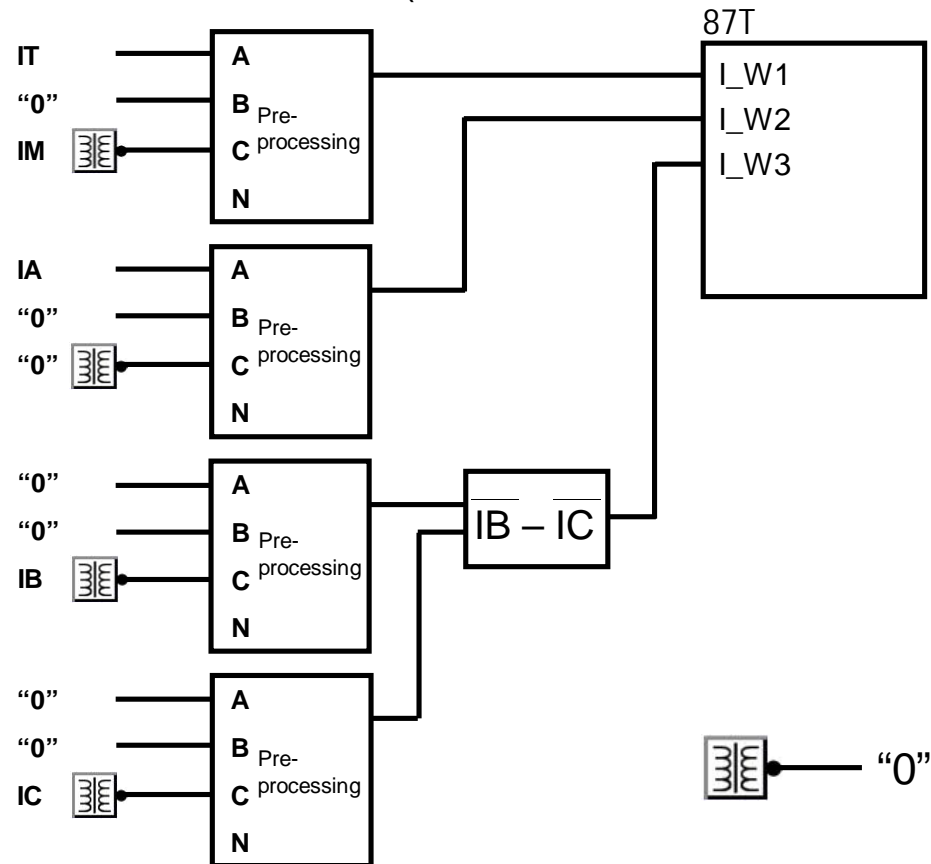
# Scott transformer

- Connection of currents to the 87T function (autotransformer shared between two track sections)



# Scott transformer

- Rated values

W1	$S_{R1} = \frac{S}{2}$	$V_{R1} = V_{LV}$	$I_{R1} = \frac{S}{2 \cdot V_{LV}}$
W2	$S_{R2} = \frac{S}{2}$	$V_{R2} = \frac{\sqrt{3}}{2} \cdot V_{HV}$	$I_{R2} = \frac{S}{\sqrt{3} \cdot V_{HV}}$
W3	$S_{R3} = \frac{S}{2}$	$V_{R3} = \frac{1}{2} \cdot V_{LV}$	$I_{R3} = \frac{S}{V_{HV}}$

- Typical settings

Rated Voltage W1	$V_{R1}$
Rated Voltage W2	$V_{R2}$
Rated Voltage W3	$V_{R3}$
Rated Current W1	$I_{R1}$
Rated Current W2	$I_{R2}$
Rated Current W3	$I_{R3}$
Connect Type W1	Delta (D)
Connect Type W2	Delta (D)
Connect Type W3	Delta (D)
Clock Number W2	0 (0 deg)
Clock Number W3	0 (0 deg)
ZS Current Subtraction W1	Off
ZS Current Subtraction W2	Off
ZS Current Subtraction W3	Off

# Scott transformer

- Example

Scott transformer


$S = 90\text{MVA}$

$S_{R1} = S_{R2} = S_{R3} = 45\text{MVA}$

$V_{R1} = 55\text{kV}$

$V_{R2} = 133.4\text{kV}$

$V_{R3} = 77\text{kV}$

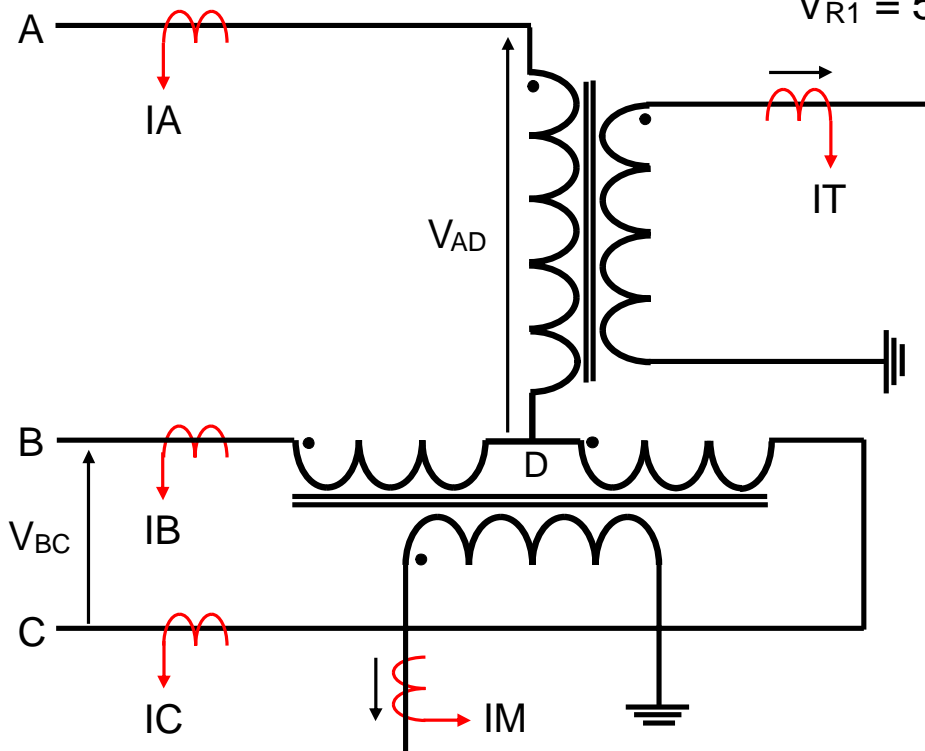

$$|V_{BC}| = |V_{HV}|, V_{BC} = |V_{HV}| \angle 0^\circ$$

$$|V_{AD}| = \frac{\sqrt{3}}{2} |V_{HV}|, V_{AD} = \frac{\sqrt{3}}{2} |V_{HV}| \angle 90^\circ$$

For  $|I_M| = |I_T| = 50\% I_{R1}$ ,  $I_M = 409.1 \angle 180^\circ$   
 $I_T = 409.1 \angle -90^\circ$

the HV-side currents are:

$$I_A = 168.7 \angle 90^\circ$$

$$I_B = 168.7 \angle -30^\circ$$

$$I_C = 168.7 \angle -150^\circ$$

$$I_B - I_C = 292.2 \angle 0^\circ$$

# Scott transformer

- Example

Scott transformer

$$\begin{aligned} \begin{bmatrix} \overline{ID\_A} \\ \overline{ID\_B} \\ \overline{ID\_C} \end{bmatrix} &= \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 409.1 \angle -90^\circ \\ 0 \\ 409.1 \angle 180^\circ \end{bmatrix} + \frac{133.4}{55} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 168.7 \angle 90^\circ \\ 0 \\ 0 \end{bmatrix} \\ &+ \frac{77}{55} * \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} * \begin{bmatrix} 0 \\ 0 \\ 292.2 \angle 0^\circ \end{bmatrix} \\ &= \begin{bmatrix} 409.1 \angle -90^\circ \\ 0 \\ 409.1 \angle 180^\circ \end{bmatrix} + \begin{bmatrix} 409.1 \angle 90^\circ \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ 409.1 \angle 0^\circ \end{bmatrix} \end{aligned}$$

## Other protections discussed in paper

---

- Restricted earthfault (87N) – split single-phase railway transformer
  - 50/51
  - 51G
  - 49
- 
- As for the 87T protection, the paper shows how to connect the analog quantities for the above protections for the different types of railway transformers

# Conclusions

---

- It has been shown how to use standard three-phase transformer protection relays to protect the most common types of 50/60Hz railway transformers
- Even though standard three-phase transformer protection relays treat the analog quantities in a three-phase manner, and this will remain so, they can be adapted and successfully applied to different types of railway transformers on 50Hz or 60Hz railway supply systems