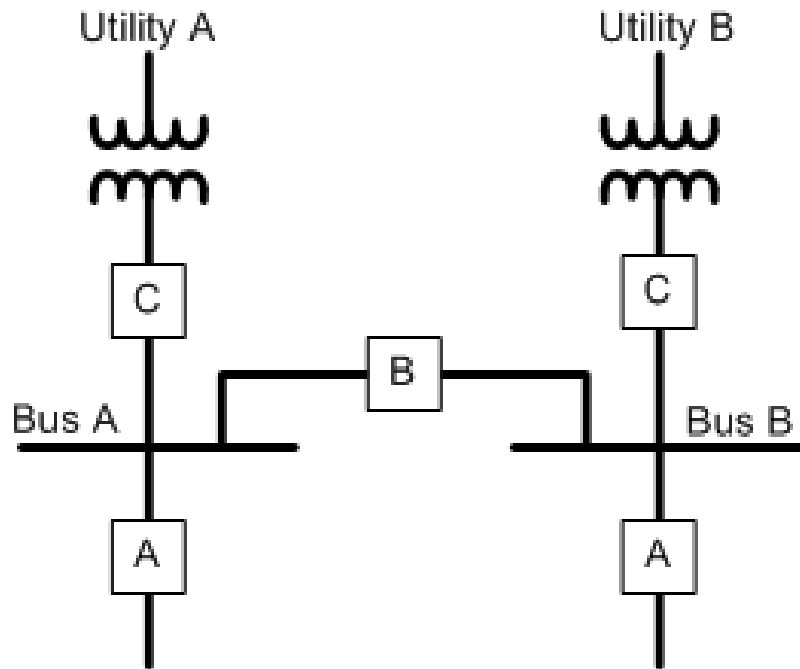




66th Texas A&M Relay Conference, April 10, 2013

# Reducing Tripping Times in Medium Voltage Switchgear

# Typical Main-Tie-Main Layout



- Tie Breaker (B) is normally open
- Tie Breaker may be closed if one transformer has failed or is being maintained

# Typical Main-Tie-Main Layout


## Three Strategies for Improving Coordination Times

- Dynamic Setting Group Change
- IEC61850 GOOSE Blocking Scheme (aka zone interlock scheme)
- Electronically Triggered Fault Current Limiter (ET-FCL)


# Typical Main-Tie-Main Layout

## Dynamic Setting Group Change

Open-Tie (Normal)

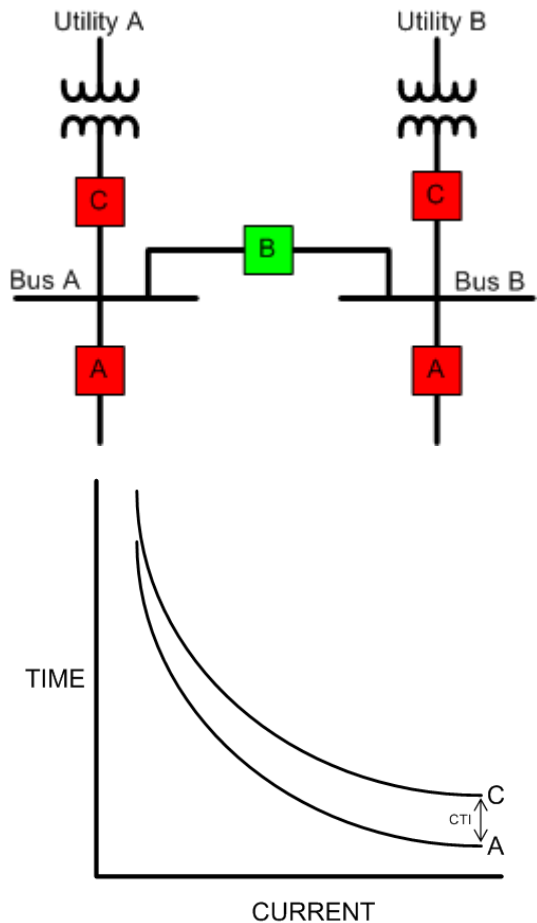


Tie-Closed (xfmr maintenance)

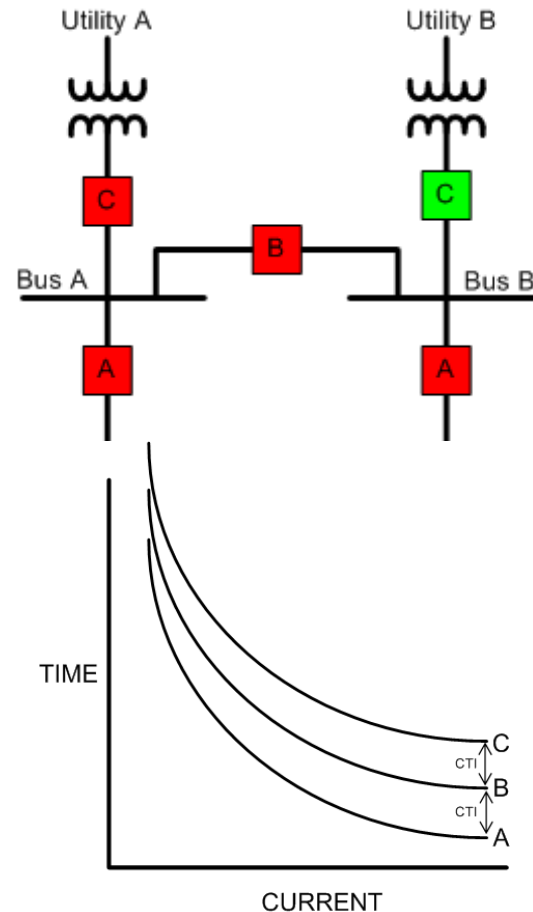

# Typical Main-Tie-Main Layout



## Dynamic Setting Group Change

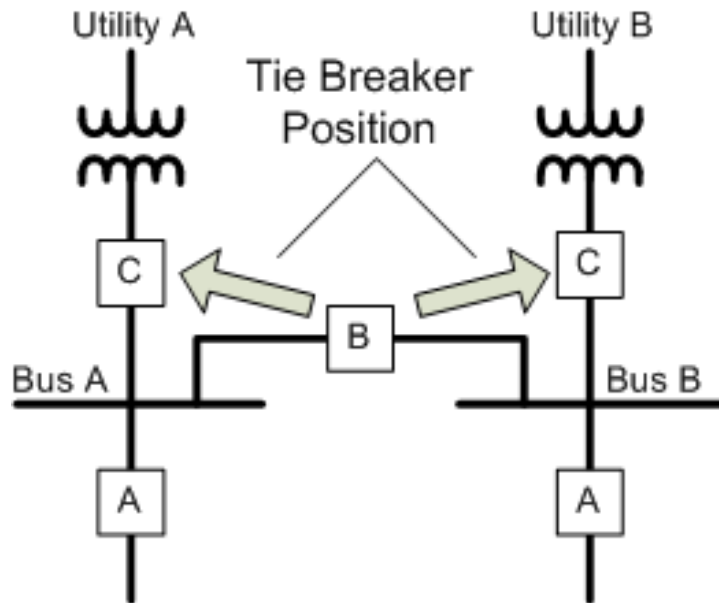


- Tie Breaker Open –  
Relay C coordinates with Relay A  
Setting Group #1 at Relay C
- Tie Breaker Closed –  
Relay C coordinates with Relay B  
Setting Group #2 at Relay C

# Typical Main-Tie-Main Layout

## Dynamic Setting Group Change

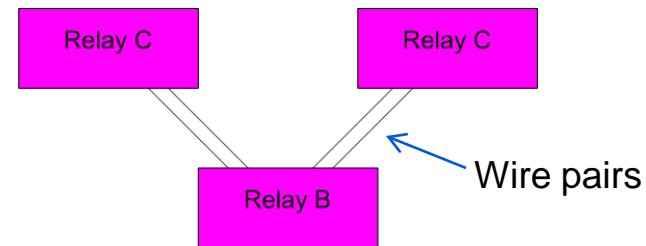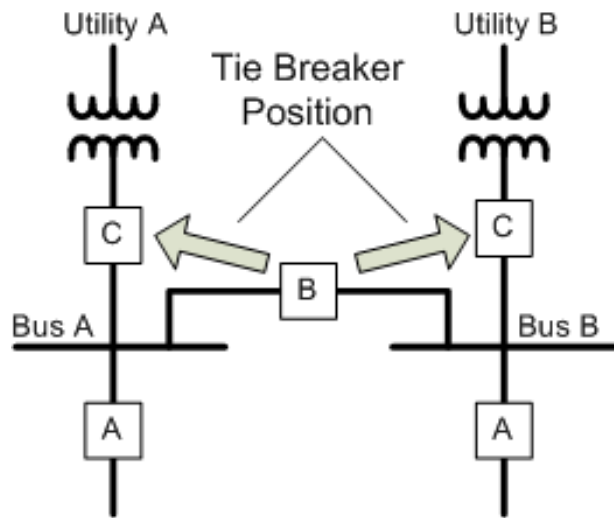

Hardwire Implementation

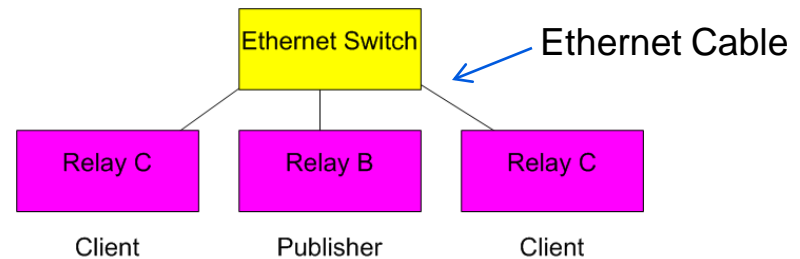


GOOSE Implementation

GOOSE = Generic Object Oriented Substation Event

# Typical Main-Tie-Main Layout
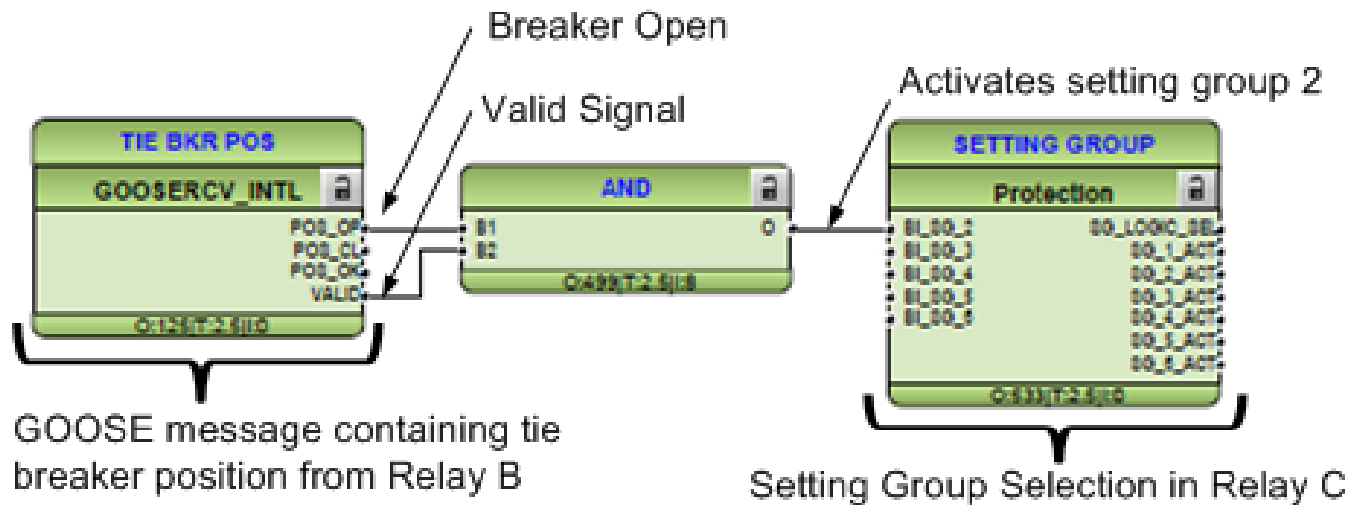
## Dynamic Setting Group Change

Typical GOOSE Implementation of Dynamic Setting Group Change Logic



# Typical Main-Tie-Main Layout



## Dynamic Setting Group Change

- Advantages
  - Simple to implement (with microprocessor relays)
  - Can be implemented with either hardwires or GOOSE (if relay supports GOOSE)
  - Improves main relay coordination 1 level
- Disadvantages
  - Hardwire connections are not typically monitored



# Typical Main-Tie-Main Layout

## IEC61850 GOOSE Blocking Scheme

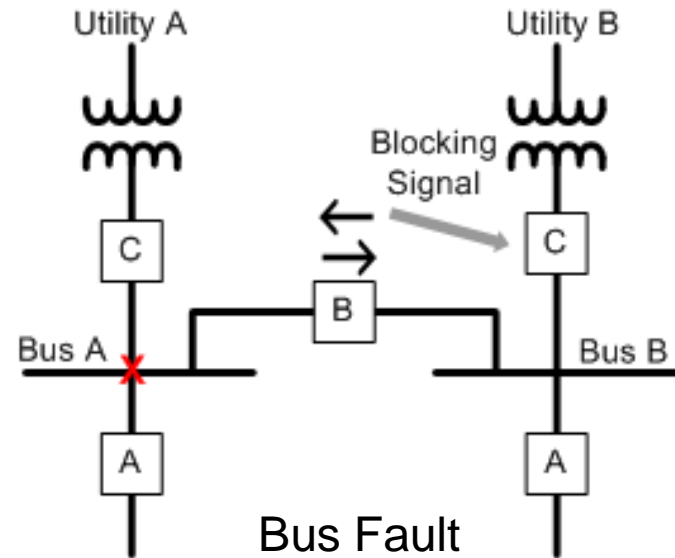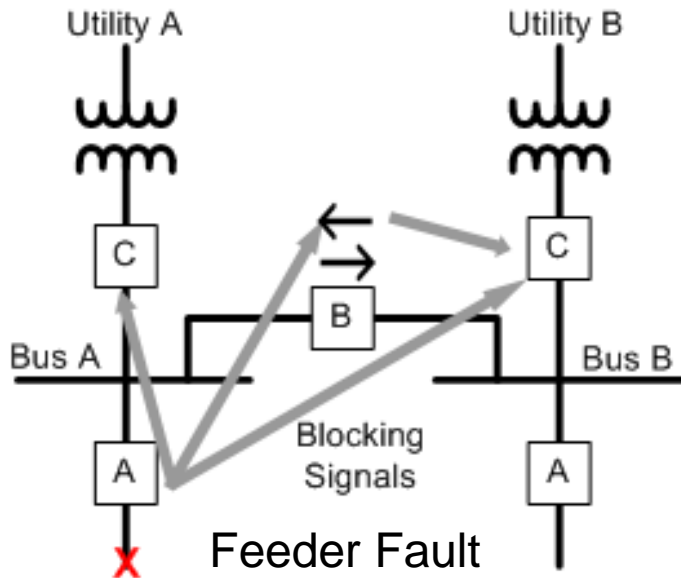


Several relays may pick up but the most downstream relay sends blocking signals upstream to temporarily prevent them from tripping.

Upstream relay inst trips are delayed about 1 cycle to allow receipt of a blocking signal. If no blocking signal is received, upstream relays are allowed to trip for fast bus fault clearing (about 2 cycles + breaker op time)


# Typical Main-Tie-Main Layout

## IEC61850 GOOSE Blocking Scheme

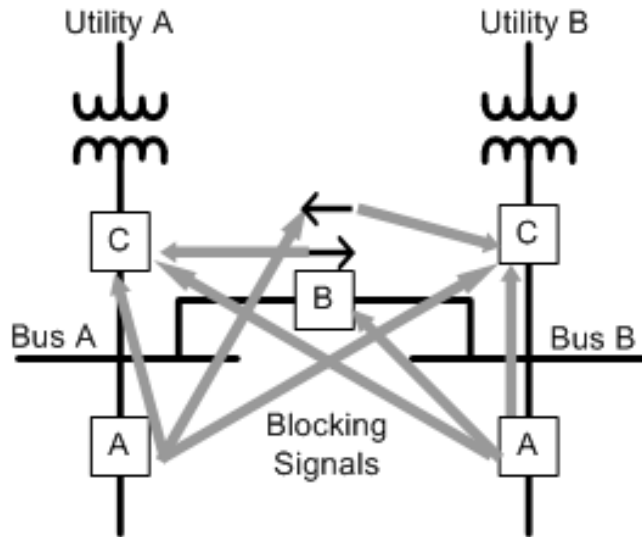
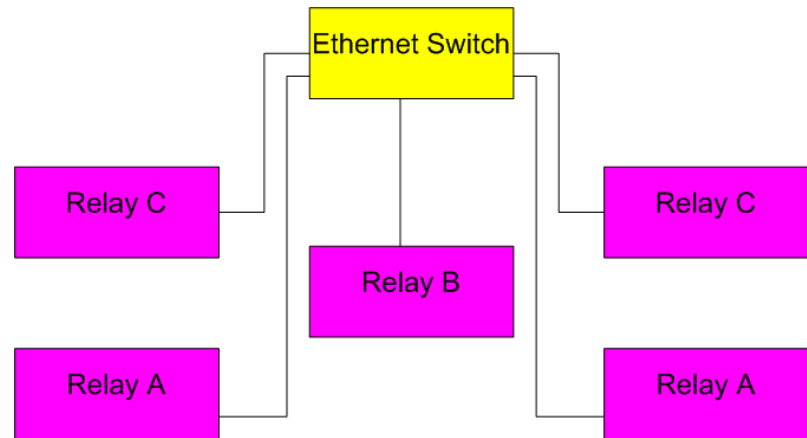
### Hardwire Implementation

- Each arrow represents a wire pair
- Each additional feeder adds 3 wire pairs
- Communication paths are not monitored
- Typical blocking delay is 5+ cycles




### GOOSE Implementation

- Single Ethernet connection between relays and switch
- Each additional relay adds 1 Ethernet cable
- All communication paths are continuously monitored
- Typical blocking delay is 1 cycle

# Typical Main-Tie-Main Layout

## IEC61850 GOOSE Blocking Scheme

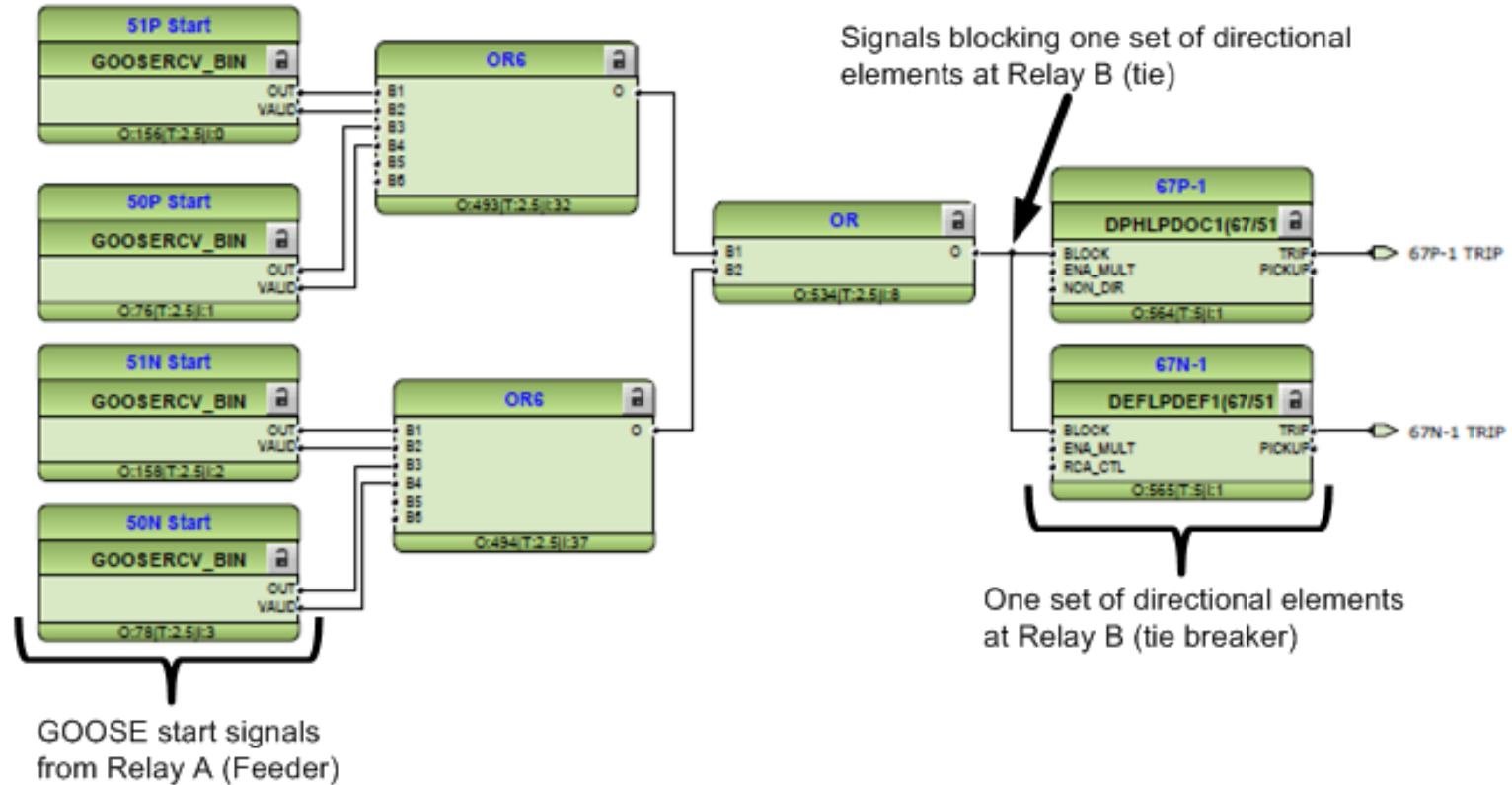

# Typical Main-Tie-Main Layout

## GOOSE Blocking Scheme

- Advantages
  - Simple physical implementation
  - Very fast operation...typically 2 cycles
  - Very little extra cost...Ethernet switch & cables
  - Eliminates time coordination. All faults can be cleared in a few cycles
  - Can be expanded to multiple levels
  - All communication paths are monitored
  - “Virtual wiring” can be copied to other relays
- Disadvantages
  - Requires IEC61850 compliant relays
  - GOOSE messaging is somewhat complex (takes practice)

# Typical Main-Tie-Main Layout


## Electronically Triggered Fault Current Limiter (ET-FCL)

- ET-FCL Characteristics
  - Ultra fast opening switch
  - Triggered to open at an adjustable “X” kA
  - Limits the first current rise in less than 1ms
  - Voltage ratings from 0.75kV to 40.5kV
  - Continuous current ratings from 630A to 5000A
  - Rated breaking current up to 210kA



# Typical Main-Tie-Main Layout
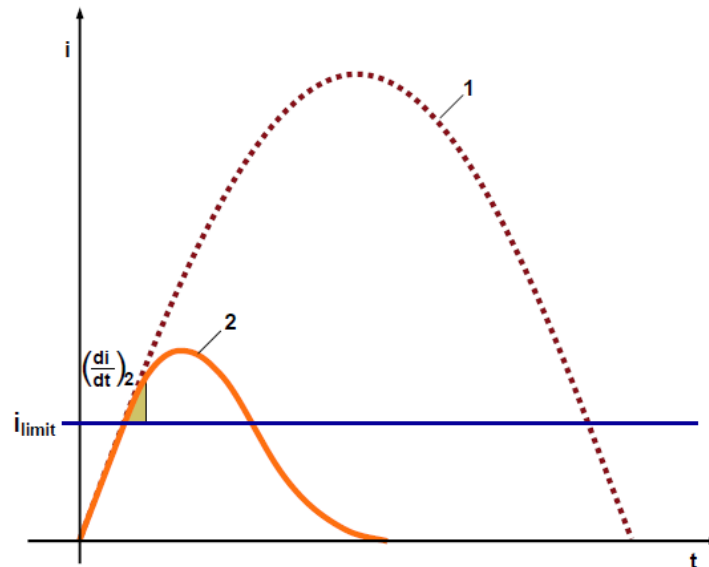
## Electronically Triggered Fault Current Limiter (ET-FCL)

- ET-FCL Characteristics
  - Triggered to trip based on  $di/dt$  slope level
  - $Di/dt$  applied to prevent false trips
  - Curve#1 is potential fault waveform
  - Interruption occurs in  $\frac{1}{4}$  -  $\frac{1}{2}$  cycle, system x/r ratio dependent



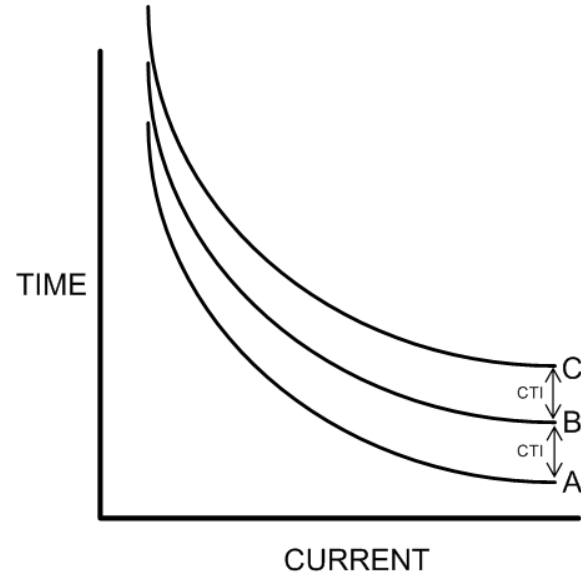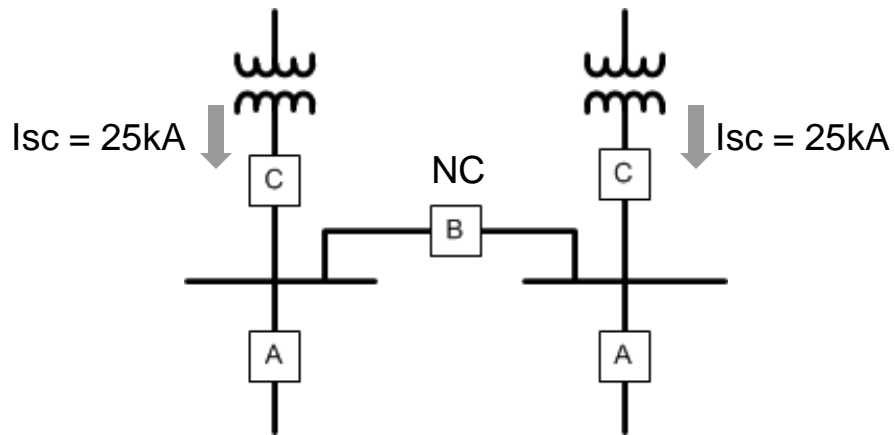
# Typical Main-Tie-Main Layout Electronically Triggered Fault Current Limiter (ET-FCL)



# Typical Main-Tie-Main Layout
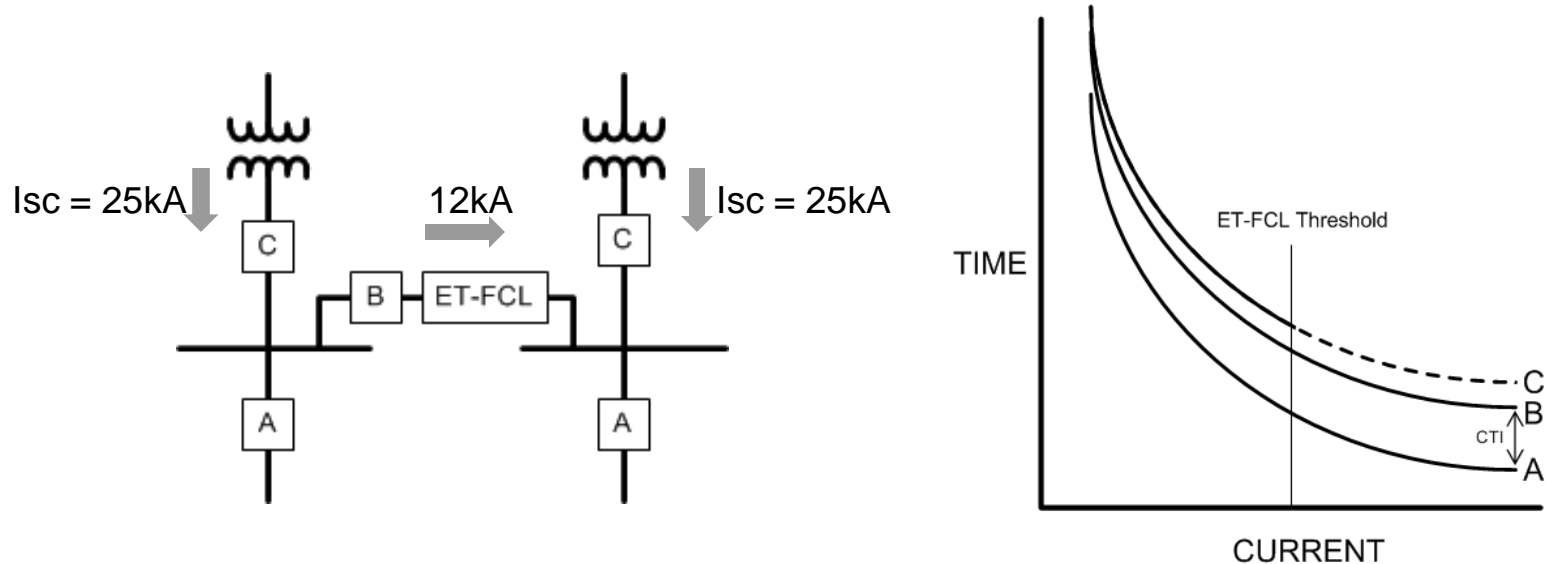
## Electronically Triggered Fault Current Limiter (ET-FCL)




- ET-FCL limits the current to its threshold setting
- Relay C only needs to coordinate with Relay B up to the ET-FCL trip value setting



# Typical Main-Tie-Main Layout
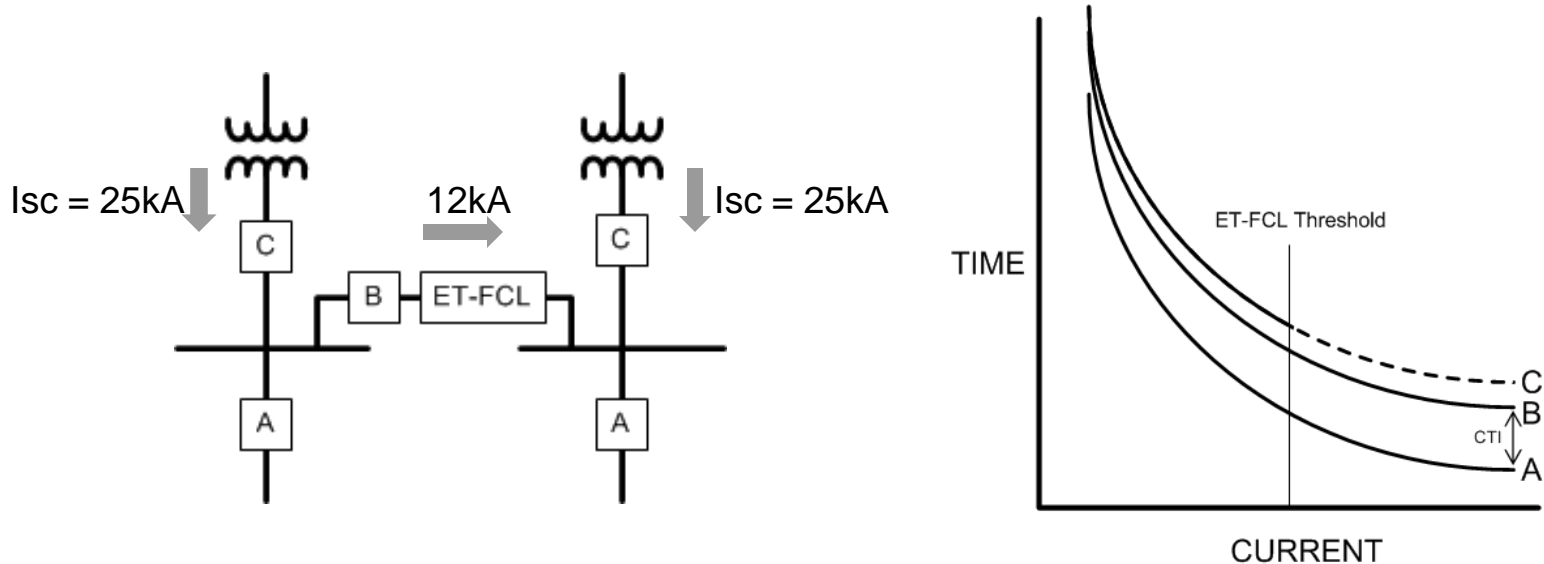
## Electronically Triggered Fault Current Limiter (ET-FCL)



- Additional ET-FCL Benefits
  - Can delay switchgear upgrades by limiting through-fault current
  - Allows buses to be tied together that otherwise would not be permitted.
  - May eliminate the need for MV motor soft starters
  - Improves voltage regulation by tying buses together

# Typical Main-Tie-Main Layout Summary

Method	Implementation	Cost	Benefits
Setting Group Change	Easy	Low	Low
GOOSE Blocking	Moderate	Low	High
ET-FCL	Difficult	High	High <sup>■</sup>

- Benefits of the ET-FCL extend beyond coordination and include many system improvements such as motor starting and delayed switchgear upgrades.